



Page NO.

1. 1 to 117 – Mid Term + Final Term

MD IFTAKHAR KABIR SAKUR

25th BATCH

COMPUTER AND COMMUNICATION ENGINEERING

International Islamic University Chittagong

COURSE CODE: CCE-1203

COURSE TITLE: Basic Electronics

COURSE TEACHER:

[Md Mostafa Amir Faisal](#)

Assistant Professor
Electronic and Telecommunication Engineering

Second

Semester

Starts From Next
page



TCCE-1203

Structure of an Atom

→ According to Bohr's theory, "the Atom consists of positively charged nucleus and a number of negatively charged electrons which revolve round the nucleus in various ~~and~~ orbits.

• According to Bohr's model, an electron is said to be moved in a orbit, whereas according quantum mechanics an electron is said to be somewhere in free space of the atom, called as orbital.

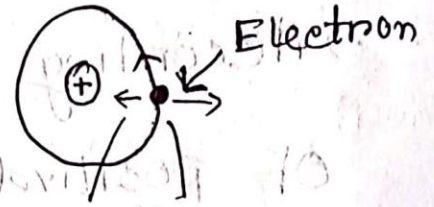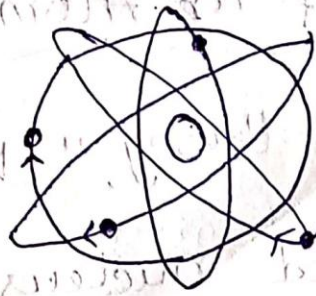A three dimensional boundary where an electron is probable to found is called as Atomic Orbital.




Electrostatic Force = centrifugal force

Valence Shell & Valence Electron:-

Electron can occupy only certain orbital rings or shells at fixed distances from the nucleus and that each shell can contain only a particular number of electrons.

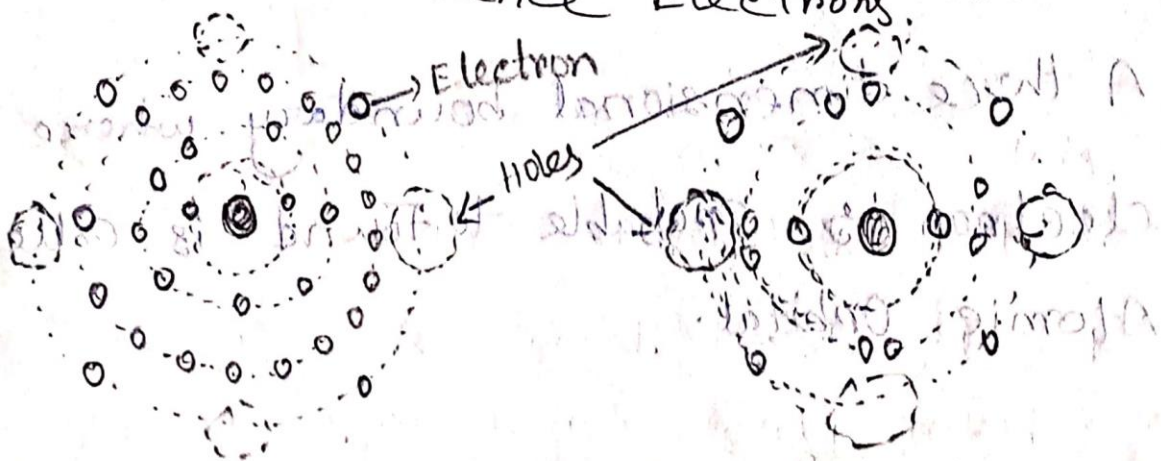The outermost shell is called valence shell and the electrons in this shell are called valence electrons.



(a) Germanium Atom

(b) Silicon Atom

Concepts of Holes -

- Each atom has a maximum of 4 electrons in their valence shell when they can contain a maximum of 8.

- It is said that, the valence shell has 4 electrons & 4 holes.

- A hole can be defined easily as an absence of an electron in a shell where one could exist.

Energy Levels

- Each shell has an energy level associated with it.

- The closer a shell is to the nucleus, the stronger are the forces that bind it.

- Energy level represents the amount of energy that would have to be supplied to extract an electron from the shell.

• Energy levels are measured in Electron volts. It is defined as the amount of Energy required to move one electron through a potential difference of one volt.

Energy Bands:

In gaseous substances, the arrangement of molecules is not close.

In liquids the molecular arrangement is moderate.

But in solids, the molecules are so closely arranged, that the electrons in the atoms of molecules tend to move into the orbitals of neighboring atoms.

• Due to intermixing of atoms in solids, instead of single energy levels, there will be bands of energy levels formed. These set of energy levels, which are closely packed are called as Energy bands.

Why should there be Energy Bands:-

Electrons carry a single electronic charge & have a spin of $\frac{1}{2}$. This implies that they are fermions, particles which obey the Pauli exclusion principle.

The Pauli exclusion principle states that two fermions can occupy the same quantum state described by a complete set of quantum numbers.

⇒ Every electron will have a specific energy associated with it.

एक-एक electron shell - व ज कक electron

शकत म कक Energy level, जतु जककुल

Energy Level मिलतु Energy Band।

band number as below is

the conduction band is the band having the

most occupied energy

Bands within Energy Band (Valence Band):-


The valence electrons in the valence shell, containing a series of energy levels, form an energy band which is called Valence Band.

- The valence electrons are so loosely attached to the nucleus that even room temperature, few of valence electrons leave the band to be free. These are called as free electrons as they tend to move towards the neighboring atoms.

- These free electrons are the ones which conduct the current in a conductor and hence called as Conduction Electrons.

- The band which contains conduction electrons is called as Conduction band.

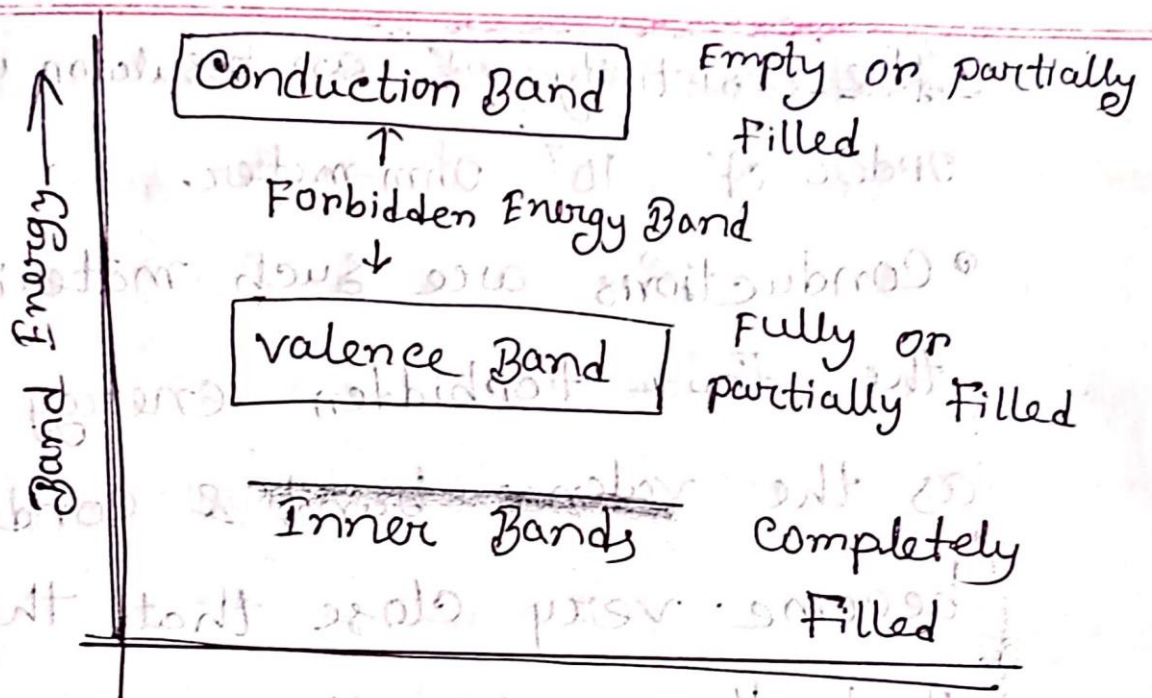The Conduction band is the band having the lowest occupied energy.



Materials according to Energy Bands (Insulator):


- Insulators are such materials in which the conduction can't take place, due to the large forbidden gap.
- Example: - wood, Rubber.
- valence band electrons are bound tightly to atoms. The value of forbidden energy gap for an insulator will be of 10 eV.
- For some insulators, as the temperature increases, they might show some conduction.

- The resistivity of an insulator will be in the order of 10^7 Ohm-meter.
- Conduction are such materials in which the ~~For~~ Forbidden energy gap disappears as the valence band & conduction band become very close that they overlap.

And there the Forbidden gap in a conductor does not exist.

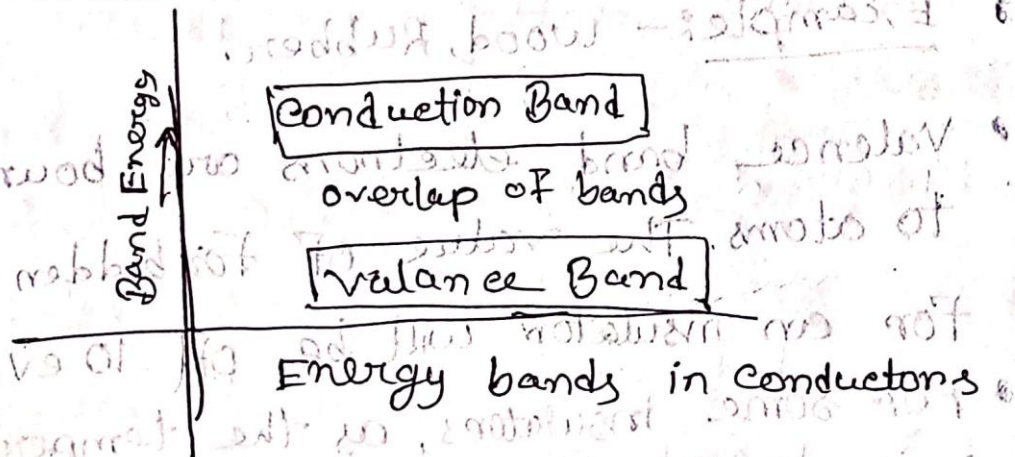Example: - Copper, Aluminum.

- A slight increase in voltage, increase the conduction.



• Semiconductors are such materials in which the Forbidden energy gap is small and the conduction takes place if some external energy is applied. The Forbidden energy gap is very small. Example:- Silicon, Germanium.

• A semiconductor is neither an insulator nor a good conductor. As the temperature increases, the conductivity of a semiconductor increases. The conductivity of a semiconductor will be in the order of 10^2 mho-meter.

अर्धचालकहरूको लागि Ohm's Law प्रयोग गर्न सकिने छ।

☐ Conduction in Semiconductors:-

• Both valence electrons combine to form "Electron pairs". This bonding is not so very strong & hence it is a covalent bond.


Example: Germanium, which has 4 valence electrons.

Covalent: - अणुसंयोजक बन्धन

Hole Current: -

When a covalent bond is broken, a hole is created. Actually, there is a strong tendency of semiconductor crystal to form a covalent bond.

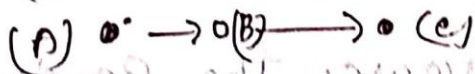• An electron, when gets shifted from a place, a hole is formed.



एवं Flow के तमाम इस hole current

⇒ This movement of hole in the absence of an applied field is random. But, when electric field is applied, the hole drifts along the applied field, which constitutes the hole current.

This is called hole current but not electron current, because the movement of holes contributes the current flow.

Temperature এর effect velocity এর উপর
electron এর অধিকার এর উপর নহে।

Conductor এ যত temperature বাড়বে তত বেশ
Current এর Flow।

→ Due to the thermal energy supplied to the
Crystal, some electrons tend to move out
of their place & break the covalent bonds.
These broken covalent bonds, result in free
electrons which wander randomly. But the
moved away electrons creates an empty space
or valence behind, which is called as a hole.

- The hole is a unit positive charge
& electron is a unit negative charge. The liberated
electrons move randomly but when some external
electric field is applied, these electrons move in
opposite direction to the applied field.

But the holes created due to absence of
electrons, move in the direction of applied field.


Temperature coefficient কমাতে \otimes resistance
এর জন্য কমাতে হয়

Negative Temperature Coefficient:-

* Temp. বাড়লে electron এর সংখ্যাও উন্নত হলে effect আছে না বরং এর flow এর উন্নত effect আছে।

* Semiconductor Material এর ক্ষেত্রে temp. বাড়লে current এর flow বেড়ে যায়।
Resistance এর মান কমে যায়।

Semiconductor's classification

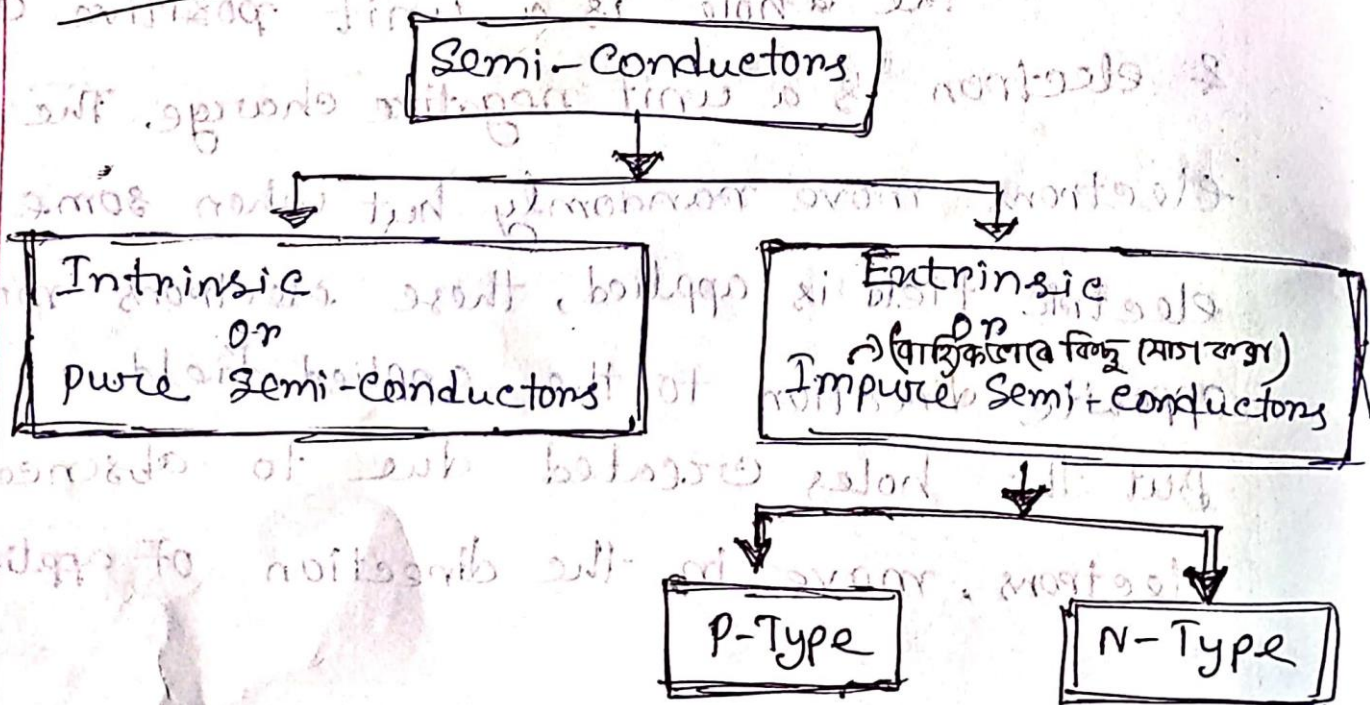

13th February, 2021

Saturday

Intrinsic Semiconductor

(अशुद्धता रहित- पदार्थ)

→ A semi-conductor in its extremely pure form is said to be an intrinsic semiconductor. The electrons & holes are created by thermal excitation. The number of free electrons is equal to the number of holes. The conduction capability is small at room temperature.

Extrinsic Semiconductor

(अशुद्धता सहित- पदार्थ)

In order to increase the conduction capability of intrinsic semiconductor, it is better to add some impurities. This process is called as Doping.

This doped intrinsic semi-conductor is called as an Extrinsic Semiconductor.

There are two types of impurity:-

1) Pentavalent Impurities:-

→ (पञ्चमानी) → 5 valence electron

The pentavalent impurities are the ones which has five valence electrons in the outer most orbit.

The pentavalent atom is called as donor atom, because it donates one electron to the conduction band of pure semi-conductor atom. Example:- Bismuth, Antimony, Arsenic,

Phosphorus.

2) Trivalent Impurities:-

→ (त्रिमानी)

The ones which has three valence electrons in the outer most orbit.

It is called as an acceptor atom because it accepts one electron from the semiconductor atom.

Example:- Gallium, Indium, Aluminum, Boron.

N-Type Extrinsic Semiconductor:-

(Access electron \rightarrow n -type Semiconductor material \rightarrow N-type semiconductor material \rightarrow)

\Rightarrow A small amount of pentavalent impurity is added to a pure semiconductor to result in N type extrinsic semiconductor.

The added impurity has 5 valence electrons.

Example:- IF (As) atom is used to the (Ge) atom, four of the valence electrons get attached with the (Ge) atoms while one electron remains as a free electron.

All these free electrons constitute electron current. When, the impurity added to pure semiconductor provides electrons for conduction. As the conduction takes place through electrons, the electrons are majority carriers & the holes are minority

carriers.

• When an electric field is applied to an N-Type semiconductor, to which a pentavalent impurity is added, the free electrons travel towards positive electrode. This is called as a negative on N-type conductivity.

P-Type Extrinsic Semiconductor


A small amount of trivalent impurity is added to a pure semiconductor to result in p-type extrinsic semiconductor.

The added impurity has 3 valence electrons.

If Boron atom is added to the germanium atom, three of the valence electrons get attached with the Ge atoms, to form three covalent bonds. But one more electron in germanium

remains without forming any bond.

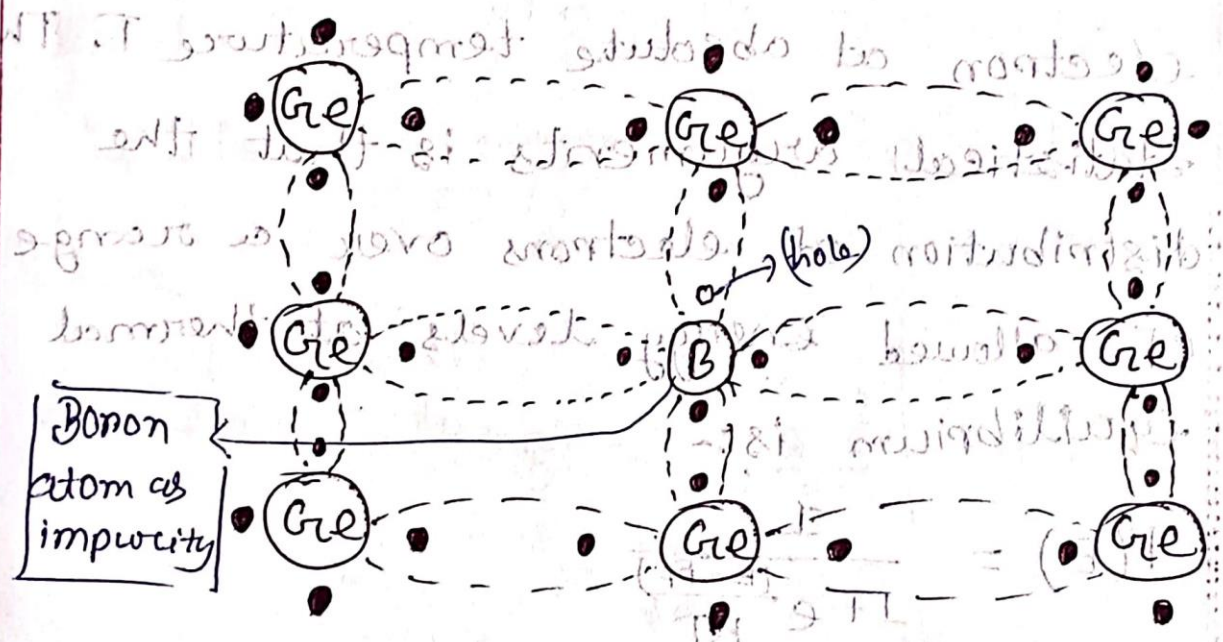As there is no electron in Boron remaining to form a covalent bond, the space is treated as a hole.



There is a constant $k = 8.6 \times 10^{-5} \text{ eV/K}$
 or $k = 1.38 \times 10^{-23} \text{ J/K}$
 The quantity E is called the Fermi energy.
 $T = \text{temperature}$

Fermi Density of States and Fermi Dirac Function:-

The function $F(E)$ is

The probability that an available energy state at E will be occupied by an electron at absolute temperature T . The

statistical arguments is that the distribution of electrons over a range of allowed energy levels at thermal equilibrium is:-

$$F(E) = \frac{1}{1 + e^{\frac{E - E_F}{kT}}}$$

Here,

k is Boltzmann's constant ($k = 8.62 \times 10^{-5} \text{ eV/K}$)

or, $k = 1.38 \times 10^{-23} \text{ J/K}$

The quantity E_F is called the Fermi level.

T = Temperature

Fermi Level

এটা এমন একটি state, যে state এ electron
 থাকার probability 50-50.

Cause,

$E = E_F$ হলে,

$$f(E_F) = \frac{1}{1 + e^{\frac{(E_F - E_F)}{k \cdot T}}} = \frac{1}{1 + e^0} = \frac{1}{1 + 1} = \frac{1}{2}$$

when,

$T = 0$

& $E > E_F$

then,

$$f(E) = \frac{1}{1 + e^{\frac{+}{0}}} = \frac{1}{1 + e^{\infty}} = \frac{1}{1 + \infty}$$

$$= \frac{1}{\infty} = 0$$

For the Fermi Dirac distribution function $f(z) = 0$.

when,

$E < E_F$

then,

$$f(z') = \frac{1}{1 + e^{\frac{-}{0}}} = \frac{1}{1 + e^{-\infty}} = \frac{1}{1 + 0} = 1$$

$$= \frac{1}{1 + 0} = \frac{1}{1} = 1$$

$f(z') = 1$.


□ Fermi Level Conduction & valence band

এই মাধ্যমে থাকে।

It means কোনো Temperature দেওয়া নাহলে

Intrinsic semi-conductor এর ক্ষেত্রে কোনো


electron পাওয়ার সম্ভাবনা নেই।

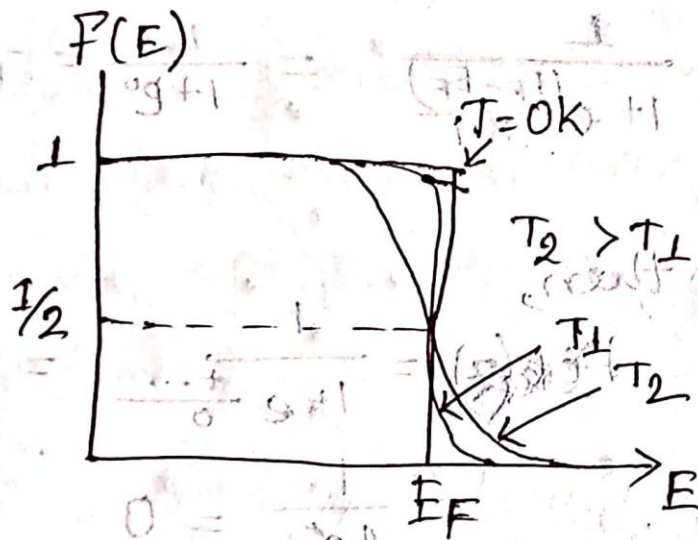


Ex:- The Fermi Dirac Distribution Function.

□ Fermi Dirac Dist. Applied to Semiconductor

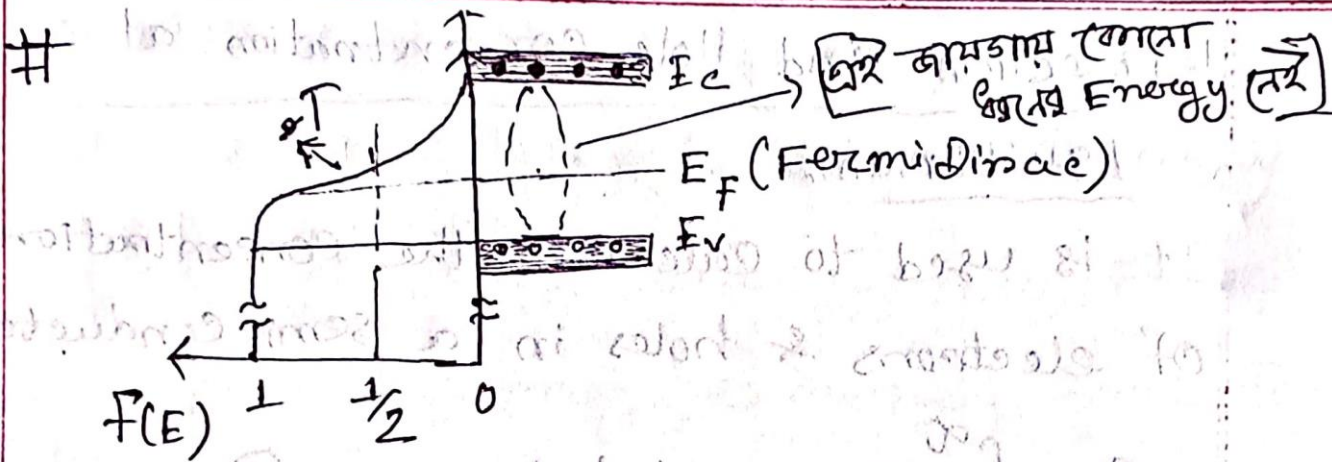
Intrinsic - এই ক্ষেত্রে Conduction Band এ
 থাকে electron আর valence Band এ
 থাকে hole থাকবে।



(a) Intrinsic

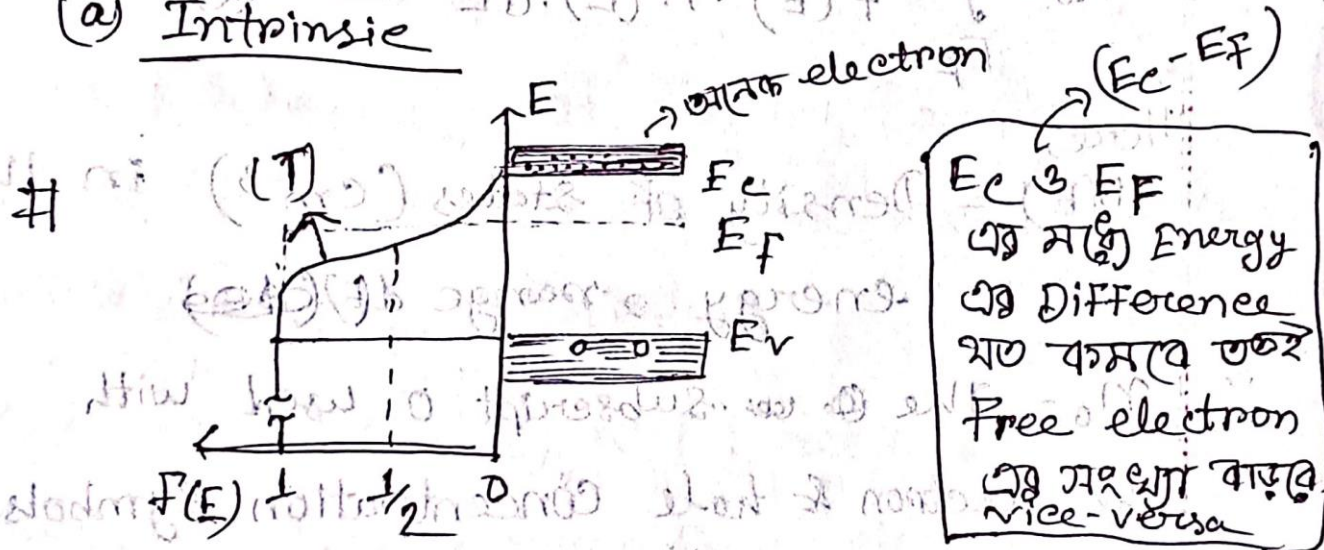

(b) n-type

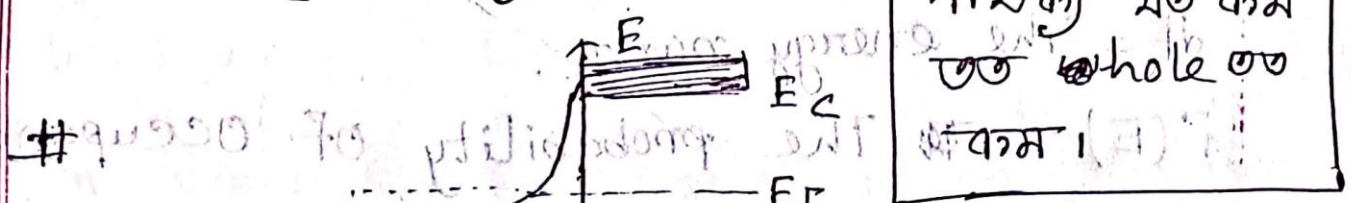

(c) p-type

The value of $E_c - E_f$ gives a measure of n (electron concentration).

The value $(E_f - E_v)$ indicates how strongly p-type material is.

Electron and Hole Concentration at Equilibrium:-

It is used to calculate the concentrations of electrons & holes in a semiconductor

$$n_0 = \int_{E_F}^{\infty} F(E) \cdot N(E) \cdot dE \quad \text{--- (2)}$$

Here,

$N(E)$ = Density of states (cm^{-3}) in the energy range dE

n_0 = The subscript 0 used with the electron & hole concentration symbols (n_0, p_0) indicates equilibrium conditions.

dE = The energy range.

$F(E)$ = The probability of occupancy.

$N(E)$ can be calculated by using quantum mechanics & the Pauli exclusion principle.


$N(E)$ is proportional to $E^{0.5}$.

The Fermi Function becomes extremely small for large energy. Also, Fermi Function becomes extremely small for large energies.

The probability of finding an empty state (hole) in the valence band $[1 - F(E)]$ decreases rapidly below E_v .

The product $F(E) \cdot N(E)$ decreases rapidly above E_c , and very few electrons occupy energy states far above the conduction band edge.

Conduction Band width (Total electron)

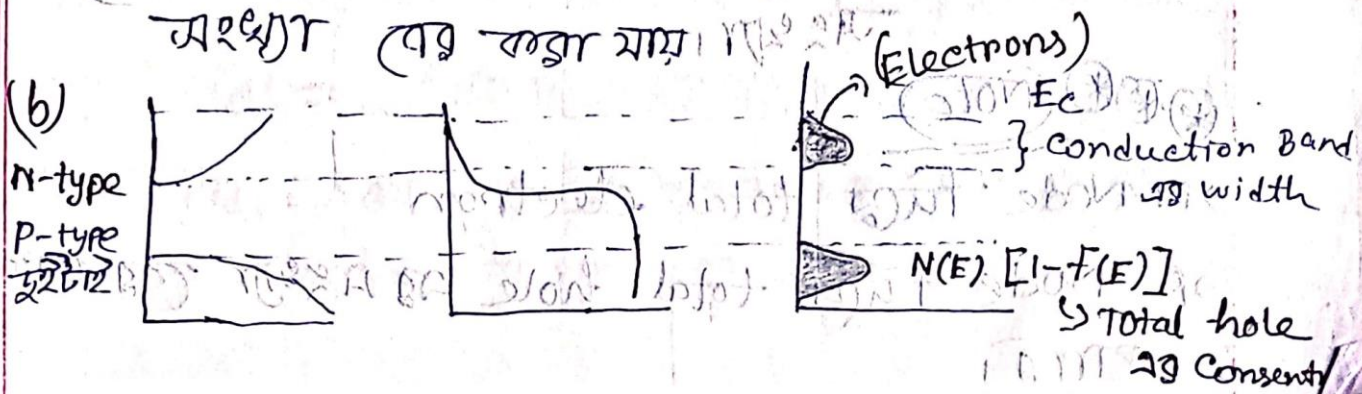

$F(E_v) =$ Occupied state probability
 অৱস্থা

□ The probability of occupancy at E_c is

$$n_0 = N_c F(E_c)$$

Here,

$N_c =$ Conduction Band এর width অক্ষর

Energy state available আছে অ

Hole এর ক্ষেত্রঃ -

$$N(E) [1 - F(E)]$$

So, The concentration of holes in the valence band is,

$$p_0 = N_v [1 - F(E_v)]$$

Here,

$N_v =$ Valence Band এর total Energy state

অ অৱস্থা

$1 - F(E_v) =$ Occupied না অৱস্থা probability

অৱস্থা

Note

→ n-Node ফিল্ড total electron

→ p-Node ফিল্ড total hole অ অৱস্থা অৱস্থা

অৱস্থা

1. কোনো একটি N-type ও P-type Material কে Doping করার দ্বারা total electron Density বড় এবং Hole এর Density কতটুকু এটা বের করতে পারবে।
 উপরোক্ত সমস্যা equation গুলোর উদ্দেশ্য।
 কারণ এর উপর Depend করে Conductivity বের করা যায়। অর্থাৎ কে কতটুকু Current conduct করতে পারে তা বের করা যাবে।

$$\Rightarrow f(E_c) = \frac{1}{1 + e^{(E_c - E_F)/KT}} \approx e^{-(E_c - E_F)/KT}$$

So, we get,

$$n_0 = N_c e^{-(E_c - E_F)/KT} \quad \text{--- (2)}$$

(Total electron)

Total available effective density of states,

$$N_c = 2 \left(\frac{2\pi m_n kT}{h^2} \right)^{3/2}$$

যদি N_c , E_c ও E_F দেওয়া থাকে তবে কোনো Material এর কয় electron সংখ্যা বের করা সম্ভব।

P-type का, $n_i = p_i$ का कारण है।

$$1 - F(E_v) = 1 - \frac{1}{1 + e^{(E_v - E_f)/KT}}$$

$$= e^{-(E_f - E_v)/KT}$$

Cause, $E_v < E_f$ है।

Intrinsic Semi-conductor का electron

का कारण -

$$n_i = N_c e^{-(E_c - E_f)/KT}$$

$$p_i = N_v e^{-(E_f - E_v)/KT} \quad (5)$$

The product of n_0 & p_0 at equilibrium

$$n_0 p_0 = (N_c e^{-(E_c - E_f)/KT}) \cdot (N_v e^{-(E_f - E_v)/KT})$$

$$= N_c \cdot N_v \cdot e^{-(E_c - E_v)/KT}$$

$$= N_c \cdot N_v \cdot e^{-E_g/KT} \quad (6)$$

अर्थात् constant temperature -

n & p का सुनता always constant है।

P-Type का,

$$1 - F(E_v) = 1 - \frac{1}{1 + e^{(E_v - E_f)/kT}}$$

$$= e^{-(E_f - E_v)/kT}$$

Cause,
 $E_v < E_f$

Intrinsic Semi-conductor का electron

का सूत्र:-

$$n_i = N_c e^{-(E_c - E_f)/kT}$$

$$p_i = N_v e^{-(E_i - E_v)/kT}$$

The product of n_0 & p_0 at equilibrium,

$$n_0 p_0 = (N_c e^{-(E_c - E_f)/kT}) \cdot (N_v e^{-(E_f - E_v)/kT})$$

$$= N_c \cdot N_v \cdot e^{-(E_c - E_v)/kT}$$

$$= N_c \cdot N_v \cdot e^{-E_g/kT}$$

अर्थात् (काला) Constant Temperature - 4

n & p का गुणक always constant रहता है

N N

$$n_i p_i = (N_c e^{-(E_c - E_i)/KT}) \cdot (N_v e^{-(E_i - E_v)/KT})$$

$$= N_c \cdot N_v e^{-E_g/KT} \quad \text{--- (7)}$$

□ Electron conductivity of a metal:-

The actual relation is $v = \mu_e E$

কোনো electric field দিলে electron কি পরিমাণ move করে তার মান

Let, $e =$ electron charge (coulomb)

$v =$ velocity of electron

$$I = n A q v$$

$A =$ cross section Area

$q =$ charge of electron

$v =$ velocity

$n =$ Amount of total electron

or, $I = n e A \mu_e E$

[কোনো জয়েন্ট মণ্ডি দিয়ে মাওয়া total current]

Also, $E = \frac{V}{l}$ (V = voltage)

$$R = \frac{V}{I} = \frac{I}{A} \left(\frac{l}{ne\mu_e} \right) = \rho \cdot \frac{l}{A}$$

So, resistivity, $\rho = \frac{1}{ne\mu_e}$; Ohm-m

Conductivity, $\sigma = ne\mu_e$; Siemens/m

Conductivity of Intrinsic Semiconductors

p_i = Density of holes in an Intrinsic Semi-conductor (per m^3)

e = electron charge (Coulomb)

A = Cross-section of the semiconductor (m^2)

Since in an Intrinsic Semiconductor,

$$n_i = p_i$$

$$I = n_i e (v_e + v_h) A$$

$$= n_i e (\mu_h + \mu_e) EA$$

Here, μ_e = electron mobility = v_e/E

μ_h = hole mobility = v_h/E

So, we $I = n_i e (\mu_e + \mu_h) A V / l$

$$\frac{V}{I} = \frac{l}{A} \cdot \frac{1}{n_i e (\mu_e + \mu_h)} = \rho_i \cdot \frac{l}{A}$$

So, resistivity of semiconductor,

$$\rho_i = \frac{l}{n_i e (\mu_e + \mu_h)} \text{ Ohm-m}$$

The electrical conductivity which is the reciprocal of resistivity is given by,

$$\sigma_i = n_i e (\mu_e + \mu_h) \text{ S/m}$$

#

So, current density $J = I/A$

$$\therefore J = n_i e (\mu_e + \mu_h) E = \sigma_i \cdot E$$

$$\therefore \sigma_i = J/E \quad \left[\begin{array}{l} \text{Current density} \\ \text{Ohm's law} \end{array} \right]$$

So, Conductivity of semiconductors depends on two factors

(i) number of current carriers present per unit volume.

(ii) The mobility of the current carriers.

Conductivity of Extrinsic Semiconductors:
(অর্থাৎ, মৌলিক Material এর ক্ষেত্রে)

$$\sigma = (n_e \mu_e + p_e \mu_h) E$$

Here, n_e = Number of electrons

μ_e = Mobility of electrons

p_e = Charge of holes

μ_h = Mobility of holes

(a) N-type Extrinsic semi-conductor:

$$\sigma_n = e(n_n \mu_e + p_n \mu_h) E$$

(b) P-type

$$\sigma_p = e(n_p \mu_e + p_p \mu_h) E$$

✓ But, N-type Materials- n electron এর সংখ্যা hole এর সংখ্যা হতে অনেক অনেক বেশি।

$$n_n \gg p_n$$

So, we can write,

$$J_n = n_n e \mu_e E$$

$$\sigma = n_n e \mu_e$$

& in

$$J_p = p_p e \mu_h E$$

$$\sigma_p = p_p e \mu_h$$

Drift:-

Semiconductor মে কারণ Flow করে current এর কারণ হলো- Drift current বান

- (i) charge electron (voltage source connect করা মাত্র electron ও hole এর movement)
- (ii) ~~low~~ voltage source connect হলে automatically বেশি হওয়া মোট কম হওয়া কারণে current এর Flow।

- * Charge drift under the influence of applied electric field
- * Diffusion of charge from a region of high charge density to one of low charge

density.

* Current Density due to hole diffusion:

=> Current Density due to hole diffusion,

$$J_h = -e D_h \frac{dp}{dx}$$

$D_h =$ electron & hole
diffusion constant

Current Density due to electron diffusion:-

$$J_e = e D_e \cdot \frac{dn}{dx}$$

e शर्त Charge,
 $= 1.6 \times 10^{-19}$

$\frac{dn}{dx}$ or $\frac{dp}{dx}$
 = Charge Carrier Density कि शर्त
 परिवर्तन शर्त

Combined Drift & Diffusion Currents:-

be Drift

$$J_e = \underbrace{e \mu_n E}_{\text{Drift current}} + \underbrace{e D_e \frac{dn}{dx}}_{\text{Diffusion current}} \text{ A/m}^2$$

$$J_h = e \mu_h P E = e D_h dP/dx \text{ Am}^{-2}$$

Drift current

Diffusion current

Relation Between D & μ

$$\mu_e = \frac{e}{kT} \cdot D_e$$

$$\mu_h = \frac{e}{kT} \cdot D_h$$

or, $\frac{D_e}{\mu_e} = \frac{D_h}{\mu_h} = \frac{kT}{e} = \frac{T}{11,600}$

This relationship is known as Einstein equation,

$t = 23^\circ\text{C}$, $T = 300^\circ\text{K}$

$D/\mu = 300/11,600 = 1/39$ or, $\mu = 39D$

Recombination

The process is essentially the return of a free conduction electron to the valence band (and vice versa) accompanied by the emission of energy.

Apart from drift and diffusion, a third phenomenon which occurs in semiconductors is called recombination. That result from the collision of an electron with a hole.

Math Solutions

51.10] Silicon is doped with acceptor atoms to a density of 10^{22} m^{-3} . If it is assumed that all acceptor centres are ionized, calculate the conductivity of the extrinsic silicon. Given that, intrinsic density is $1.4 \times 10^{16} \text{ m}^{-3}$; $\mu_e = 0.145 \text{ m}^2/\text{Vs}$ and $\mu_h = 0.05 \text{ m}^2/\text{Vs}$.

Ans: - (It is N-type material)

The minority carrier density can be found

From $n_p = n_i^2$

$$\text{Now } p = \frac{10^{22}}{1.4 \times 10^{16}} = 7.14 \times 10^5 \text{ m}^{-3}$$

$$\text{So } n = 1.96 \times 10^{10} / \text{m}^3$$

Now, to calculate the charge density ρ we use the formula

$$\rho = n_e \cdot A_e + p_e \cdot A_h$$

$$= 1.96 \times 10^{10} \times 0.145 \times 1.6 \times 10^{-19} + 10^{22} \times 0.05 \times 1.6 \times 10^{-19}$$

$$= 80 \text{ C/m}$$


(Ans)

Diode

~~P-N-type~~ It is a single piece of a semiconductor material half of which is doped by p-type impurity and the other half by N-type impurity.

The plane which dividing the two zones is called junction. The P-N

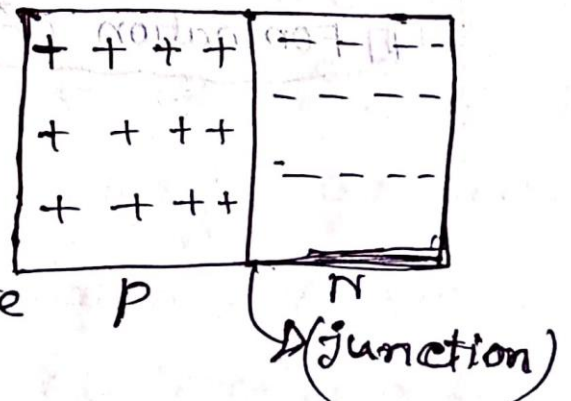junction is fundamental to the operation of diodes, transistors & other solid-state devices.



IF anything unusual happens at the junction.

It is found that three phenomena

take place:-

→ (संज्ञा कर्ता)

1] A thin depletion layer or region (also called space-charge region or transition region)

is established on both sides of the junction and is so called because it is depleted


of free charge carriers. Its thickness


is about 10^{-6} m.

2] A barrier potential or junction potential is developed across the junction.

3] The presence of depletion layer gives rise to junction ^{capacitance} & diffusion ^{→ (संज्ञा कर्ता)} capacitance.

Formation of Depletion Layer:-

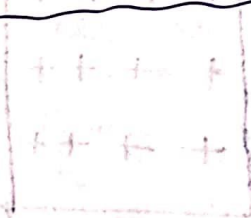

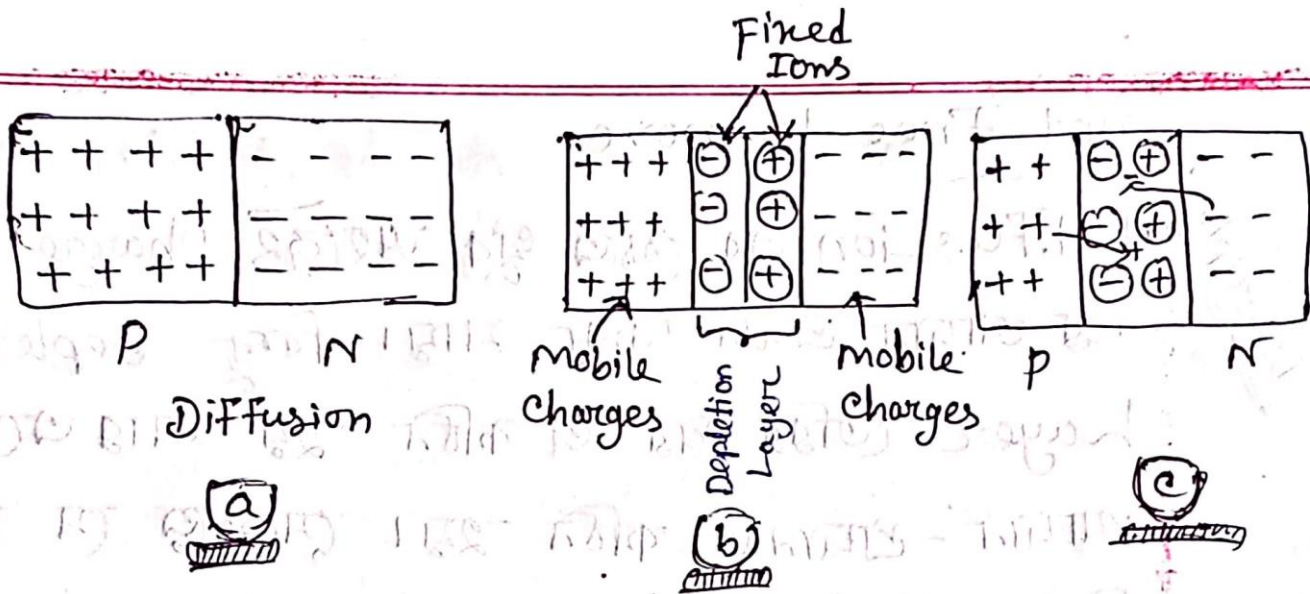

⇒ Holes are in p-region & electrons are in n-region. However, there are greater concentration of holes in p-region than in n-region. Concentration of electrons is greater in n-region than in p-region (where they exist as minority carriers).

This difference establishes density gradient across the junction resulting in carrier diffusion. So, Holes diffuse from p to n-region & electrons from n to p-region & terminate their existence by recombination. Free & mobile charge carriers like electrons & holes there being present only positive ions which are

not free to move.

• Diffusion এর ক্ষেত্রে ধ্রুব অর্ধক্রেই charge ও hole এর আদান প্রদান করা যায়। কিন্তু Depletion layer তৈরি পর অর্ধক্রেই "ধ্রুব" আর এদের আদান-প্রদানও কঠিন হয়। সেগুলো সে বিবেচনা নিয়ে আদান প্রদান করে তাকে Barrier potential বলে।

Barrier potential এর করার মাত্রা-

Silicon এর ক্ষেত্রে p-n জংশন এর B.P হলো: 0.7V

Germanium " " " " " " B.P " : 0.3V

(Room-Temperature)

এই Barrier potential কোনো Charge Flow করতে দিবে না।

Summary:

(i) Diffusion.

(ii) Depletion.

(iii) No flowing of charge.

(-) → Acceptor atom

(+) → Donor atom

□ Hole & electron এর মাঝে atom এর পারস্পরিক


চর্ক Carrier সূত্রা move করতে পারে,

atom সূত্রা move করতে পারেনা।

□ Reverse Bias:-

উদাহরণস্বরূপ NO Applied
Bias ($V_D = 0$ V) এর
অবস্থায়

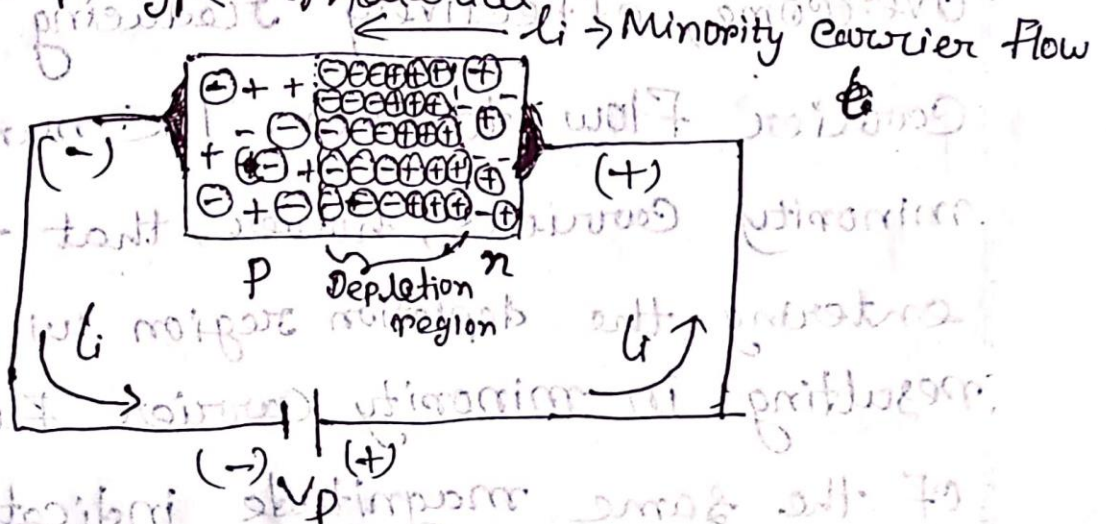If an external potential of V volts is applied across the p-n junction such that positive terminal is connected to the n-type material & the negative terminal is connected to the p-type material.



The number of uncovered positive ions in the depletion region of the n-type material will increase due to the large number of "Free" electrons drawn to the positive potential of the applied voltage.

For similar reasons, the number of uncovered negative ions will increase in the p-type material.


The net effect, therefore, is a widening of the depletion region. The widening of the depletion region will establish too great a \bar{E} barrier for the majority carriers to overcome, effectively reducing the majority carrier flow to zero. The number of minority carriers, however, that find themselves entering the depletion region will not change, resulting in minority carrier flow vectors of the same magnitude indicated with no

applied voltage:

The current that exists under reverse-bias conditions is called the reverse saturation current & is represented by I_v .

Minority current এর Flow হওয়া ক্ষেত্রে সচরাচর Saturation.

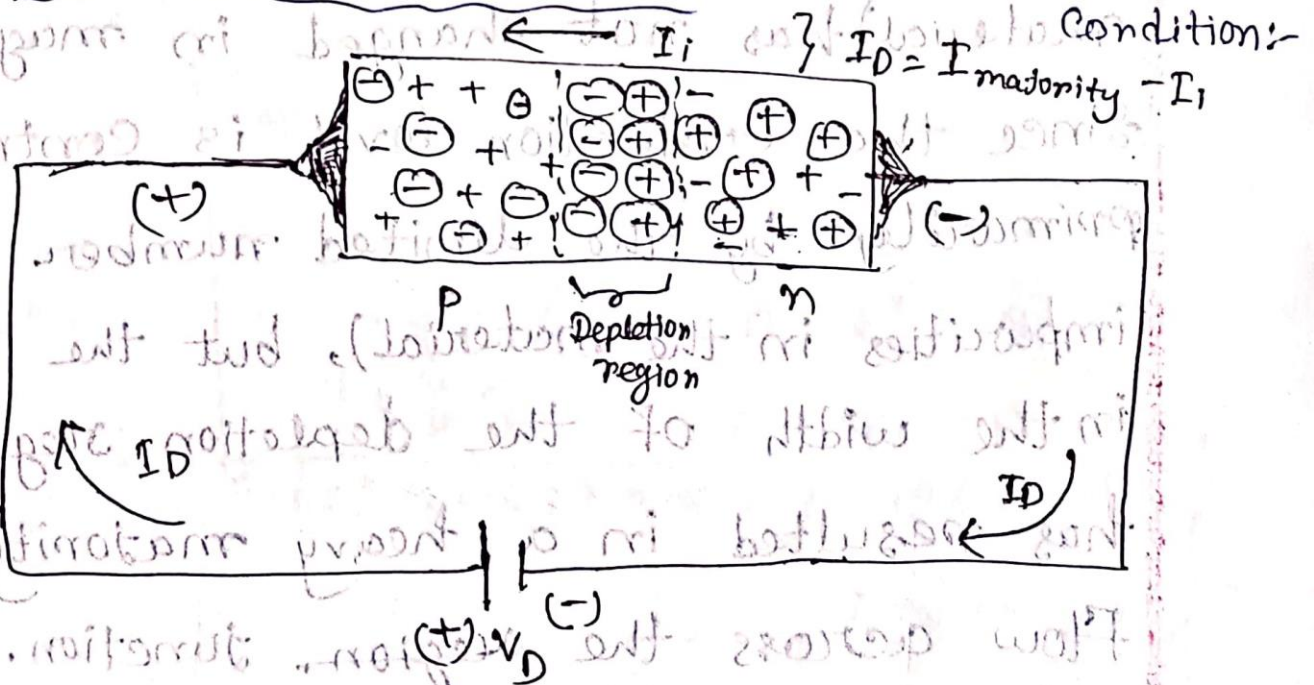
Forward-Bias Condition (সচরাচর important)



V_D will "pressure" electrons in the n-type materials & holes in the p-type material to recombine with the ions near the boundary & reduce the width of the depletion region. The resulting minority carrier flow of electrons from the p-type materials to the n-type material (and of holes from the n-type to p-type material) has not changed in magnitude. Since the conduction level is controlled primarily by the limited number of impurities in the material, but the reduction in the width of the depletion region has resulted in a heavy majority flow across the ~~region~~ junction.

An electron of the n-type material now "sees" a reduced barrier

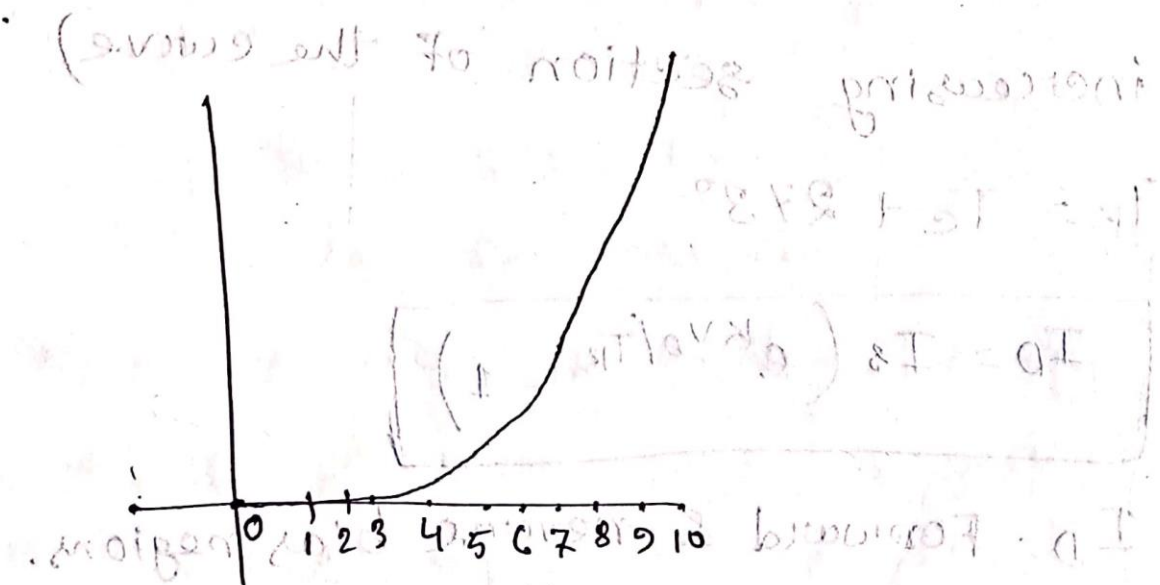at junction due to the reduced depletion region & a strong attraction for the positive potential applied to the P-type material. As the applied bias increases in magnitude the depletion region will continue to decrease in width until a flood of electrons can pass through the junction.



□ I_s = reverse saturation current

$k = 11600/\eta$ with η

$\eta = 1$ For Ge and $\eta = 2$

$\eta = 2$ For Si For relatively low

levels of diode current (at or below

the knee of the curve)

$\eta = 1$ For Ge & Si For higher level of

diode current (in the rapidly

increasing section of the curve)

$$T_k = T_c + 273^\circ$$

$$I_D = I_s \left(e^{kV_D/T_k} - 1 \right)$$

I_D = Forward & reverse bias regions.

□ Zener Regions


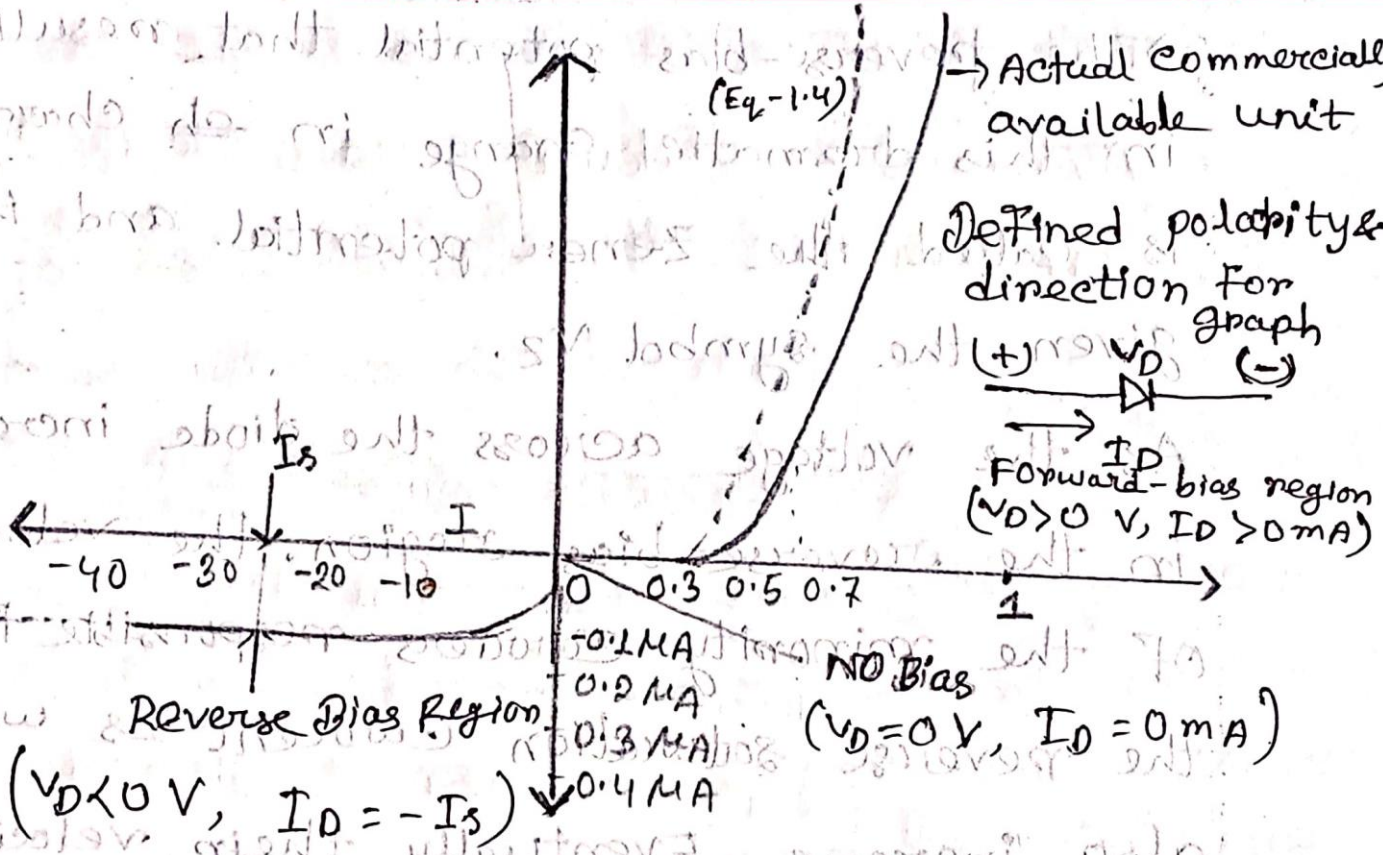


Figure 1 - Silicon semi-conductor diode characteristics

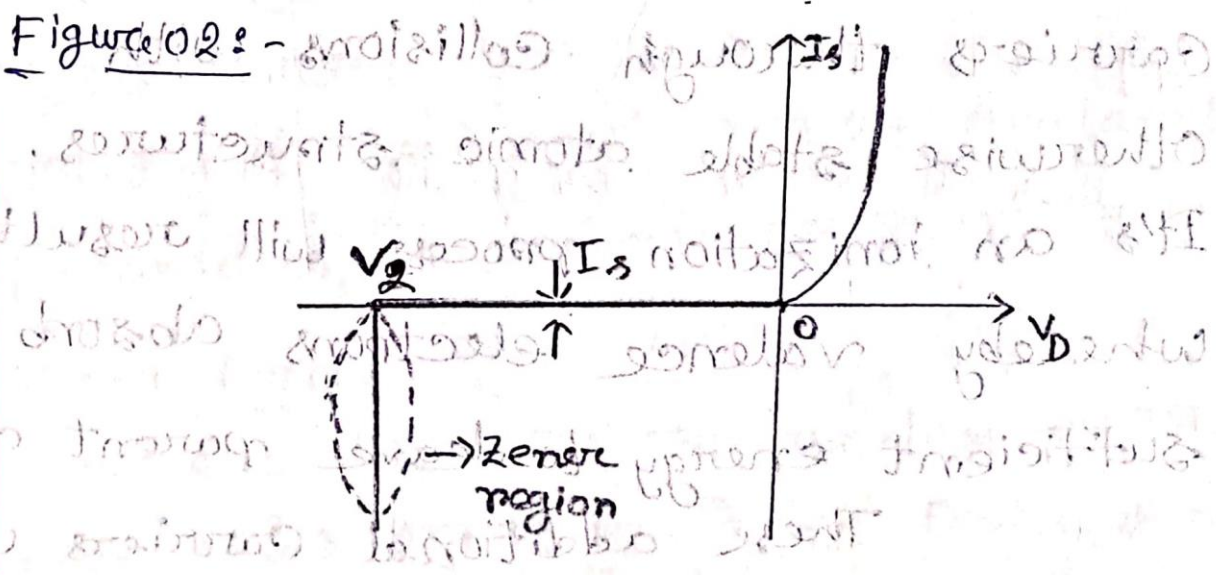

⇒ The reverse-bias potential that results in this dramatic change in characteristics is called the Zener potential and is given the symbol V_Z .

As the voltage across the diode increases in the reverse-bias region, the velocity of the minority carriers responsible for the reverse saturation current I_S will also increase. Eventually, their velocity and associated kinetic energy ($w_k = \frac{1}{2}mv^2$) will be sufficient to release additional carriers through collisions with otherwise stable atomic structures. It's an ionization process, will result whereby valence electrons absorb sufficient energy to leave parent atom. These additional carriers can

then aid the ionization process to the point where a high avalanche current is established & the avalanche breakdown region determined.

(যদিও ভোল্টেজ প্রসারের পর Reverse-bias region I_s বৃদ্ধি পায়। Minority carrier এর Reverse saturation current I_s এর কণ্ড ও বৃদ্ধি পায়। তাদের কোয় এবং ডায়নামিক স্ক্রোল মূল্য electron স্ক্রোল কোয় বৃদ্ধি পায় এবং কোয় crystal এ আঘাত করে। এর মূল্য crystal হতে electron স্ক্রোল মুক্ত অবস্থায় ছুটে আসে।

অর্থাৎ এই ঘটনাটিকে বলা হয় Avalanche Breakdown) এবং process কে বলা হয় Avalanche)

Zener Diode:-

Current Flow হবে reverse bias -এ আবার diode নষ্টও হবে না। এ ধরনের Diode কে বলা হয় Zener diode।

Note:

Avalance breakdown এর সময় Diode কে ব্যবহার করা যায় না। অর্থাৎ এই region এ কাজ করাটা ঠিক না।


PRV rating:-

এটার মানে হলো কোনো Peak Reverse voltage PRV লেখা থাকলে মানে কোনো কিছুকে Reverse Bias -এ কোনো কিছুকে অর্থাৎ voltage দেওয়া হবে এর থেকে বেশি দেওয়া হলে তা নষ্ট হতে পারে।

Diode-এ voltage বৃদ্ধি দেওয়া থাকে।

Diode এর Resistance:-

একে তিনটি ভাগে ভাগ করা হয়।

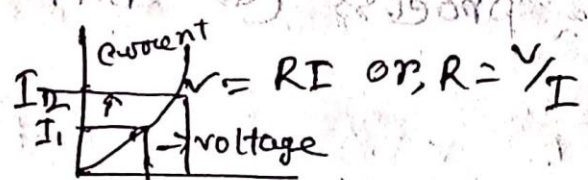


এখানে, $R = \frac{V}{I}$ এবং Diode এর ক্ষেত্রে প্রতিটি point এর Resistance value সমান না। কিন্তু Coulomb

law এর ক্ষেত্রে উভয়ই সমান।


Types- (নির্দিষ্ট voltage দেওয়া)

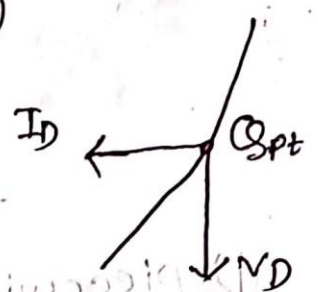(i) DC or static, $R_D = \frac{V_D}{I_D}$




(Defined as a point on the characteristics)

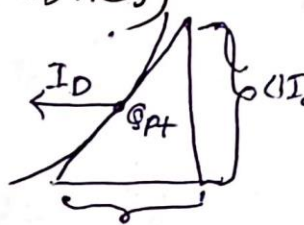(ii) AC or Dynamic, $r_d = \frac{\Delta V_D}{\Delta I_D} = \frac{26\text{mV}}{I_D}$



(Defined by a tangent line at the Q-point)

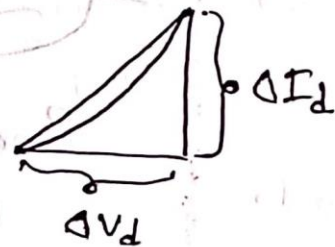(iii) Average AC, $r_{av} = \frac{V_D}{I_D}$ pt. to pt.




(Defined by a straight line between limits of operation)



[দুইটা পয়েন্টের voltage এর difference এর current difference এর ratio এর ক্রম]

২৭



Diode equivalent Circuits

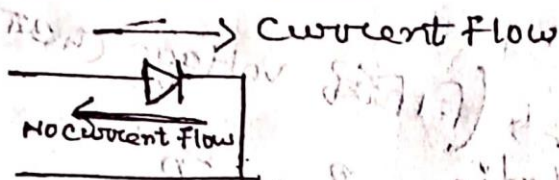



(i) Piecewise-linear Model

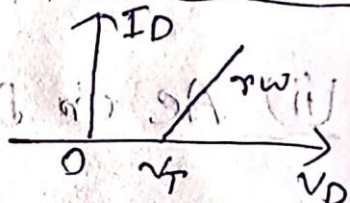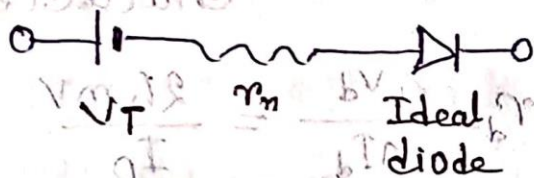

(ii) Simplified Model

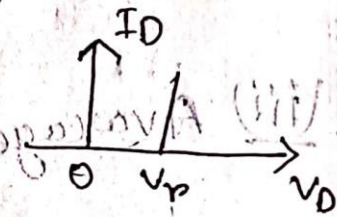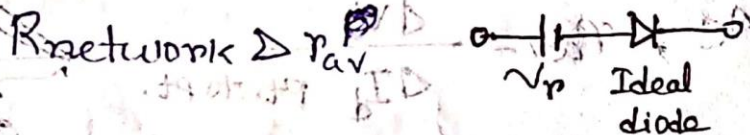

(iii) Ideal Device

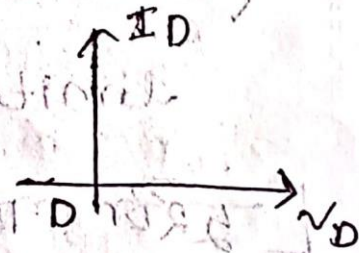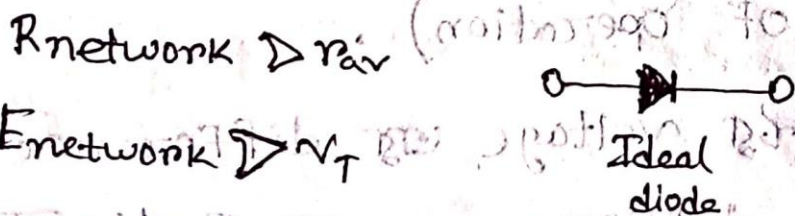

अकल Diode 0.7V एउ अकल वधि

Create करे एउटा मे अब current के flow करे कोना resistance हाउ।

Transition & Diffusion Capacitance :-

Forward Bias - এ voltage লুপার শ্রা Capacitance

এই মান তত বাড়তে থাকবে।

আর বিপরীত বায়াস

At low frequencies and relatively small levels of capacitance the reactance of a capacitor, determined by, $X_c = \frac{1}{2\pi fC}$, is usually so high that it can be considered infinite in magnitude.

In the p-n semiconductor diode, there are two capacitive effects to be considered. Both types of capacitance are present in the forward & reverse bias regions. But one so outweighs (শ্রা অতিক্রম করে) the other in each region that we consider the effect to be of only one in each region.

Capacitance of a parallel-plate capacitor is defined by, $C = \epsilon A/d$; where ϵ is the permittivity of the dielectric (insulator) between the plates of area A separated by a distance d . ~~ϵ is the permittivity of the dielectric (insulator)~~


In a diode the depletion region behaves essentially like an insulator between the layers of opposite charge.

Since the depletion width (d) will increase with increased reverse-bias potential, the resulting transition capacitance will decrease.


The capacitance is dependent on the applied reverse-bias potential has application in a number of electronic systems.

Transition (C_T), barrier, or depletion region Capacitance, is determined by,

$$C_T = \frac{C(0)}{(1 + |V_R/V_K|)^n}$$

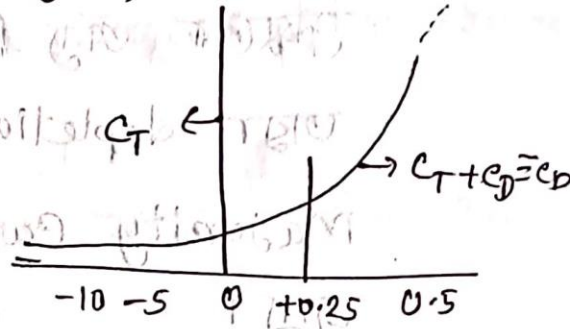

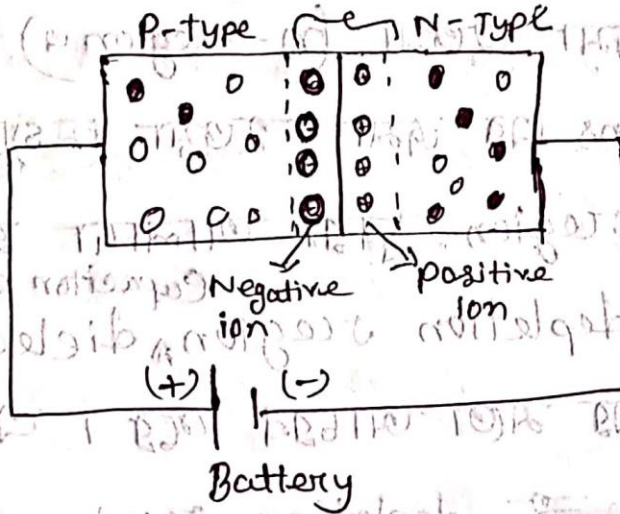সূত্রকম্পনা :- Free Electrons $\rightarrow \bullet$
Holes $\rightarrow \circ$ Depletion region



- (i) Depletion layer
- (ii) Barrier potential
- (iii) Diffusions Capacitance

Forward bias - voltage applied across P-n junction

যদি P-n junction এ প্রযুক্ত হয় তবে n- region এ free electrons OF n region will move to p-region & recombines

with the holes. একই ভাবে, p-region এ holes

n-region এ move করবে। এতে depletion region এর width কমে যায়।

elec'n - region হতে p-region এ electrons জুলা minority হয়ে যায়

একইভাবে p-region এর holes n-region এ minority হয়ে যায়। অনেক ডোনা charge carrier মেসুলো অন্য বিকিওনে মাওয়ার টাই করতে এখন তারা depletion region এ কমতে থাকবে। Majority carriers এর মাঝে recombined হওয়া কন্য।

Holes এর কমা হওয়া (n-region এ) এবং p-region এ electrons এর কমা হওয়া মেসুলো দাতা depletion region দ্বারা আলাদা হয়ে বৃদ্ধি। তারা এই depletion region, dielectric অথবা insulator এর মতো আচরণ করে। এবং ~~উপস্থিত~~ charge store-এ depletion region এর উল্লম্ব দাতা charge store হতে থাকে মেসুলো capacitor এর conducting plates এর মতো আচরণ করে থাকে।

যদি Diode এর মণ্ডি দিমে অনেক electric current flow হয় তবে অনেক charge depletion region এ কমা হয়। এবং এর ফলে অনেক বড় diffusion capacitance বর্ডে।

আবার যদি I_{current} কম থাকে তাহলে I_{current} Flow হয়
 তবু I_{current} কম হওয়ায় charge depletion region
 এ কম হয়। এর ফলে, small diffusion capacitance
 পাওয়া যায়। depletion region কম হলে diffusion
 capacitance বৃদ্ধি পায়।

The diffusion capacitance value will be
 in the range of nano farads (nF) to
 micro farads (μF).

Formula:-

$$C_D = dq/dv$$

C_D = Diffusion capacitance

dq = change in number of minority
 carriers stored outside the depletion
 region.

dv = Change in voltage applied across diode.

Impedence Infinity = open circuit

Light Emitting Diodes (LED)

LED consists Gallium Arsenide phosphide (GaAsP) or Gallium phosphide (GaP).

The process of giving off light by applying an electrical source of energy is called electroluminescence.

Math (How to solve diode math)

2.11 to 2.15 problem

$$V_b / e = q$$

$C_p = \text{diffusion capacitance}$

$q = \text{charge in number of minority}$

carriers stored outside the depletion region.


region.

$qV = \text{charge in voltage applied across diode}$

২.৭] Sinusoidal Inputs : Half - wave Rectification:-

AC হতে DC তে রূপান্তর করা হয় Rectifier।
 যা বাহ্যিক বলে একমুখীকরণ।


২ টি টার্মিনেল Rectifier রয়েছে

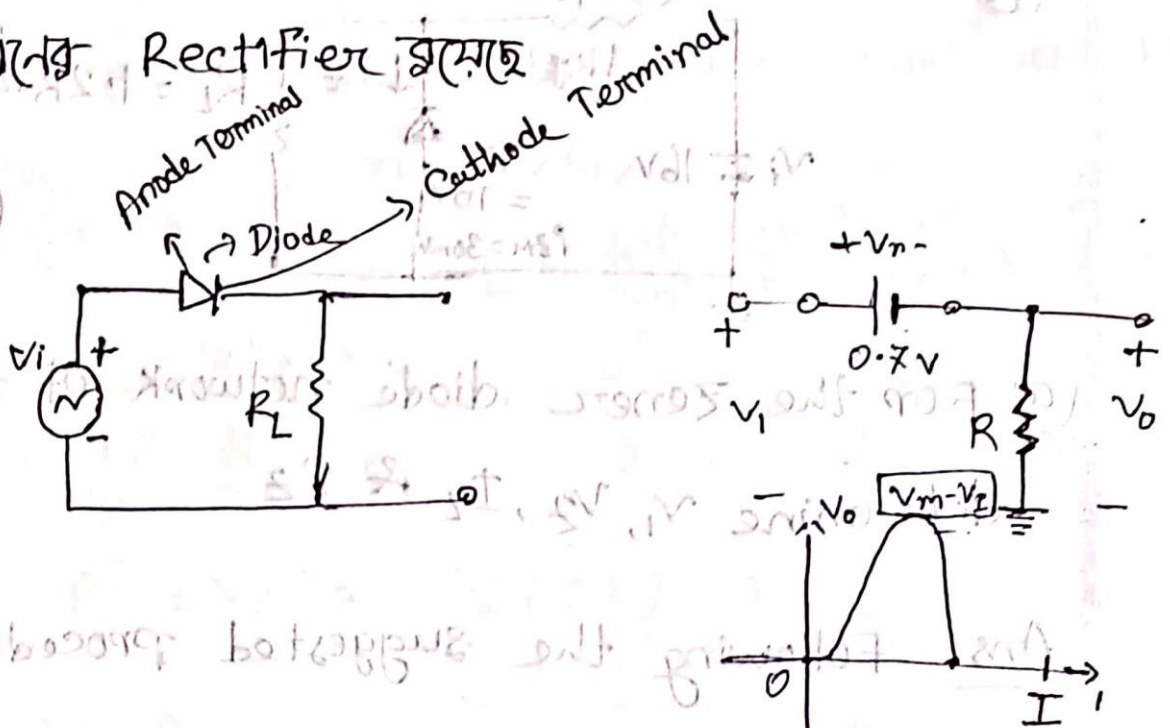

Half rectifier :-

Full - wave Rectifier :-


$$V_{dc} \approx 0.636(V_m - 2V_d)$$

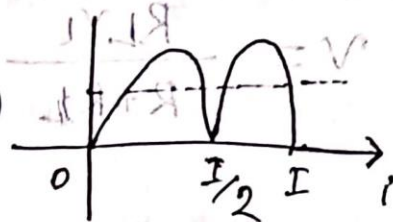

Zener Diodes:-

parallel Branch \rightarrow দুই বকম voltage रहे पावेना।

Math:-

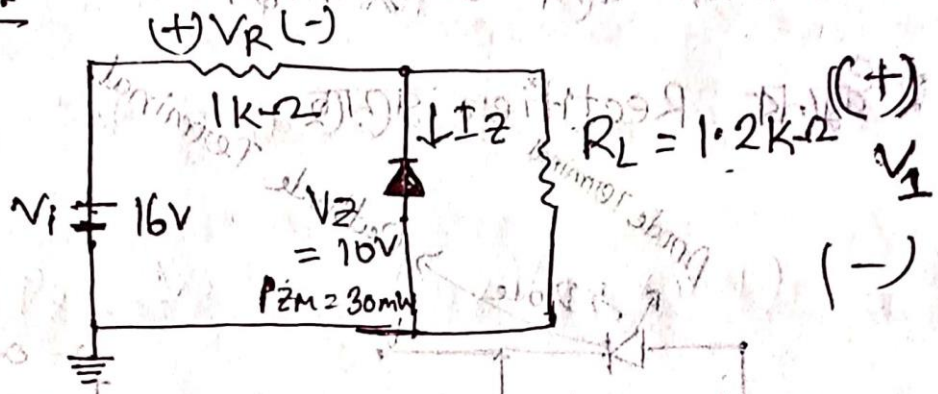

(a) For the Zener diode network of Fig 2.09 determine V_1, V_2, I_2 & P_2

Ans:- Following the suggested procedure the network is redrawn as shown in Fig

2.110 Applying Eq. (2.16) gives,

$$V = \frac{R_L V_1}{R + R_L} = \frac{1.2 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 1.2 \text{ k}\Omega} = 8.73 \text{ V}$$

(a) Repeat part (a) with $R_L = 3K\Omega$

Since $v = 8.73V$ & less than $V_Z = 10V$

so the diode is in OFF state; substituting the open-circuit equivalent will result in the same network,

$$V_L = V = 8.73V \quad \left[\text{In parallel branch the voltage can't be different} \right]$$

$$V_R = v_i - V_L = (16V - 8.73V) = 7.27V$$

$$I_Z = 0A$$

$$P_Z = V_Z I_Z = V_Z (0A) = 0W$$

(b) Here,

$$v = \frac{R_1 V_i}{R_1 + R_2} = \frac{3K\Omega \times 16V}{1K\Omega + 3K\Omega} = 12V$$

$v = 12V$ is greater than $V_Z = 10V$. So the

diode is in ON state.

$$V_L = V_Z = 10V$$

$$V_R = v_i - V_L = (16V - 10V) = 6V$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{3K\Omega} = 3.33mA$$

$$I_R = \frac{V_R}{R} = \frac{6V}{1k\Omega} = 6mA$$

$$I_Z = I_R - I_L$$

$$= 6mA - 3.33mA$$

$$= 2.67mA$$


The power,

$$P_Z = V_Z I_Z = (10V)(2.67mA)$$

$$= 26.7mW$$

which is less than specified, $P_{ZM} = 30mW$

Math:-

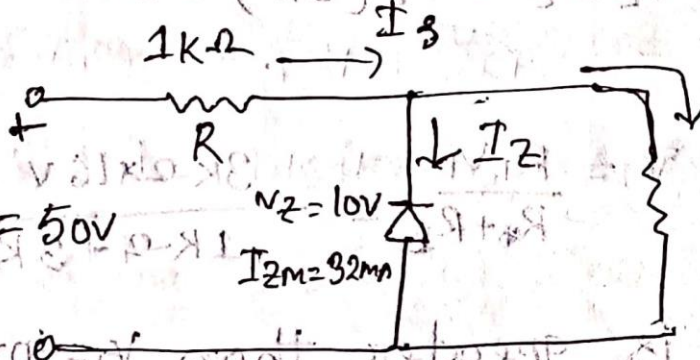

(a) For the network of this figure, determine

the range of R_L & I_L that will result in V_{RL} being maintained at 10V.

Solutions

$$V_L = \frac{R_L}{R+R_L} V_{in}$$

$$\text{or, } 10 = \frac{R_L}{1k\Omega + R_L} 20$$

$$\text{So, } R_{L\min} = \frac{1}{5} (1k\Omega + R_L)$$

$$V_{L\min} = \frac{(R_L + R) V_2}{R_L} = \frac{(1200\Omega + 220\Omega) (20V)}{1200\Omega}$$

$$= 23.67V$$

$$I_L = \frac{V_L}{R_L} = \frac{V_2}{R_L} = \frac{20V}{1.2k\Omega} = 16.67 \text{ mA}$$

$$I_{R\min} = I_{Z\min} + I_L = 60 \text{ mA} + 16.67 \text{ mA} \\ = 76.67 \text{ mA}$$


$$V_{\text{in}\min} = I_{R\min} R + V_2$$

$$= (76.67 \text{ mA}) \cdot (0.22k\Omega) + 20V$$

$$= 16.87V + 20V$$

$$= 36.87V$$

Half wave voltage :-

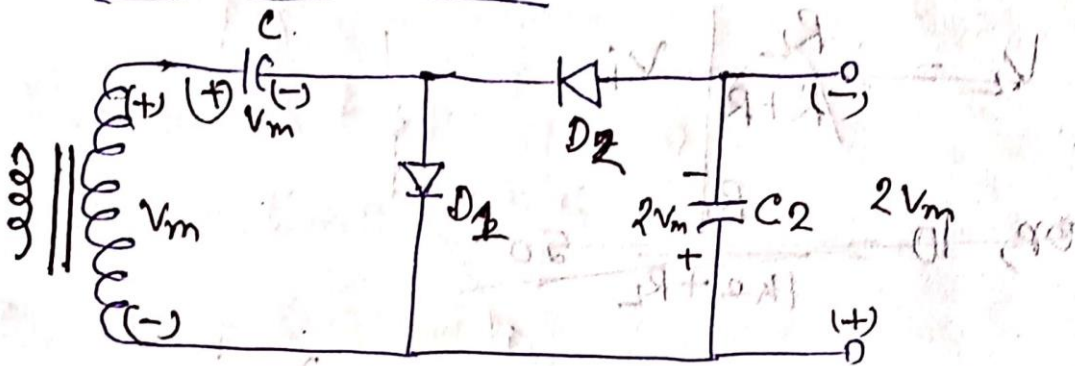

Normal Bias $\rightarrow D_1$

Reverse Bias $(+)$ $(-)$ এবং $(-)$ $(+)$ সেক্ষেত্রে D_2

Ideal Diode (Circuit explanation) :-

Forward Bias এ সে কাজ করে কিন্তু Reverse Bias এ কাজ করে না। এবং এ মাথ মাঝে 0.7 volt এর কোনো Drop নেই তাইকে Ideal Diode বলে।

$$V = IR + V_s$$

$$V_{0.5} + (0.7) \cdot (0.2) =$$

$$V_{0.5} + 0.14 =$$

$$0.64 =$$

Simple series Clippers (Ideal Diodes) :-




Signal এর একটা অংশকে স্কর্সে কেটে ফেলা বা কি অংশকে অক্ষয় রেখে এই ডিভিসিটো মে circuit এর মাধ্যমে আমরা achieve করি যে মার্কেটকে বলা হয় clipper circuit.

এখানে, চাইলে Negative/positive পার্ট থেকে স্কর্সে কেটে ফেলাও পারি। চাইলে বেশি কাটা যায় বা কম কাটা যায়।

Clipping of Signal :-

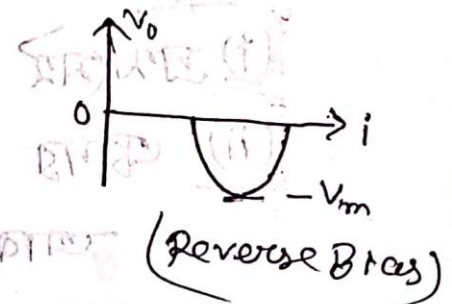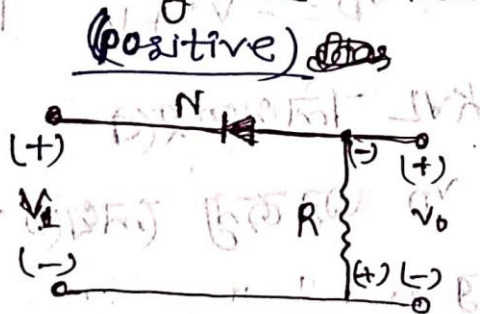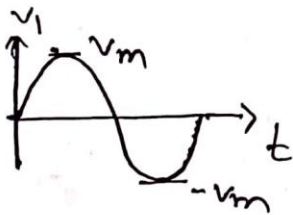(i) Simple Series Clippers (এতে বাধুতি কোনো voltage থাকে না)



এখানে positive & Negative half এ আলাদাভাবে



(iv) Diode Forward - Bias হলে V_o থাকবে

(v) মান (কিছু) বসানো কন্যু,

Negative:

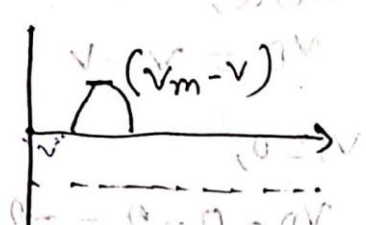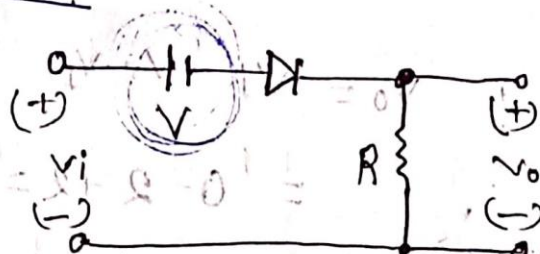

Calculations: -


$$V_F = -1$$

$$\text{So, } V_D = -V_i + V = 1 + 2 = 3$$

$$\text{So, } V_o = V_i + V_D - V = -1 + 0 - 2 = -3$$

$$\text{(ii) } V_D = -V_i + V = 5 + 2 \quad (V_i = -5)$$
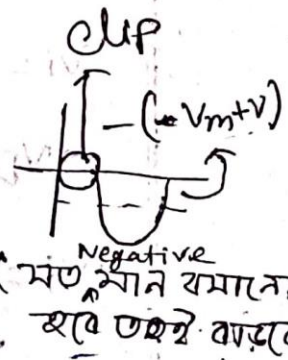
$$\text{So, } V_o = V_i + V_D - V = -5 + 0 - 2 = -7$$





Negative
(মত মান যমানো হবে তখন ব্যবে)

[V এবং V_i এর মানের পার্থক্য সত কম ধরা হবে ততই clip এর মাত্রা বেশি। (vice versa)]

[এভাবে Biasing voltage এর মাধ্যমে clip এর মাত্রা Control করতে পারা যায়]

Forward Bias এ V_D এর মান ০ হয়।

Negative:-

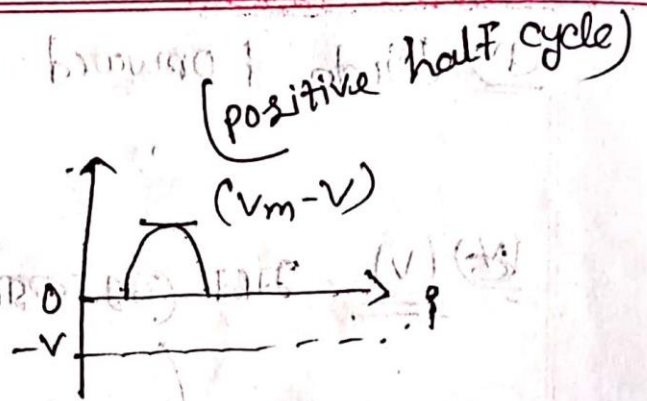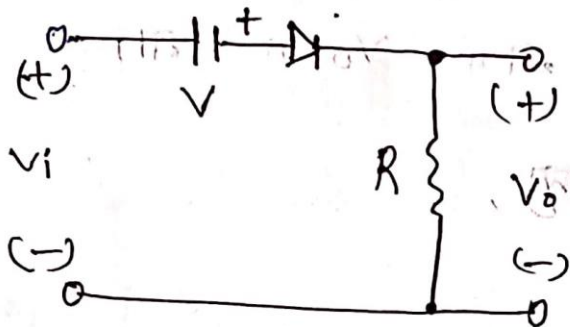

KVL,

$$-V_i + V + V_D + V_o = 0$$

Here,

$$V_D = V_i - V$$

$$V_i = 0,$$

$$V_D = 0 - 2 = -2 \text{ [V এর মান ২ গুণ]}$$

(Reverse Bias)

$$V_i = 1,$$

$$V_D = 1 - 2 = -1$$

$$V_i = 2,$$

$$V_D = 2 - 2 = 0$$

$$V_i = 3,$$

$$V_D = 3 - 2 = 1$$

$$V_i = 5,$$

$$V_D = 5 - 2 = 3$$

$$V_o = V_i - V - V_D$$

$$= 0 - 2 + 2 = 0$$


$$V_o = 1 - 2 + 1 = 0$$

$$V_o = 2 - 2 + 0 = 0$$

$$V_o = 3 - 2 - 0 = 1 \text{ [Forward Bias এ } V_D = 0 \text{]}$$

$$V_o = 5 - 2 - 0 = 3$$

Negative half cycle: iV

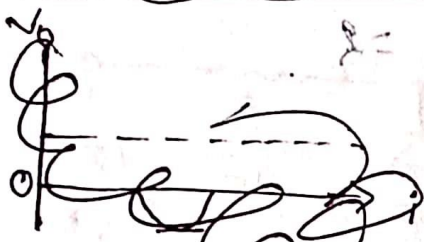

$$\Sigma = \Sigma + 0 = 0V$$

$$V_D = V_i - V$$

$$= -5 - 2$$

$$= -7$$

$$\Sigma = 0V$$

$$\Sigma + 0 = 0V$$

$$\Sigma =$$

$[V_i - V - V_D = 0V]$

$[V_i - V - V_D = 0V]$

$$\Sigma = iV$$

$$\Sigma - 0 = 0V$$


$$0 =$$

$$\Sigma =$$

$$V_i - V - V_D = 0V$$

$$= -5 - 2 + 7$$

$$= 0$$

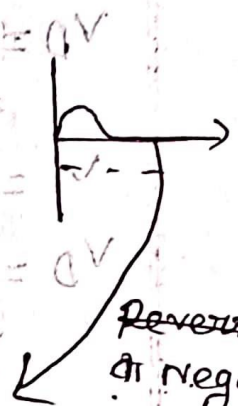

Reverse at negative

practise:-

$$\Sigma + \Sigma - = 0V$$


$$\Sigma =$$

$$\Sigma = iV$$

$$V - iV = 0V$$

$$\Sigma - 1 =$$

parallel clipper circuit

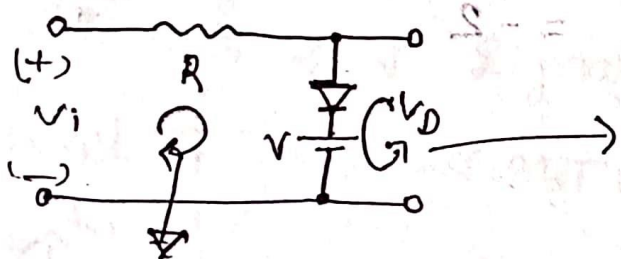

$$-V_i + V_R + V_D + V = 0$$

$$V_D = V_i - V$$

Let, $V_i = 0$ & $V = 2$

$$\text{So, } V_D = 0 - 2$$

$$= -2$$

$$V_i = 1$$

$$V_D = 1 - 2 = -1$$

$$-V_o + V_D + V = 0$$

$$\text{Or, } V_o = V_D + V$$

So,

$$V_i = 0 \text{ \& } V = 2$$

$$V_o = -2 + 2$$

$$= 0$$

$$V_i = 1$$

$$V_o = -1 + 2$$

$$= 1$$

$$V_i = 2$$

$$V_D = 2 - 2$$

$$= 0$$

$$V_i = 3$$

$$V_D = 3 - 2$$

$$= 1$$

$$V_i = 2 \text{ (input)}$$

$$V_o = 0 + 2 = 2$$

$$V_i = 3$$

$$V_o = 0 + 2 \text{ [Forward Bias]} \\ = 2$$

Negative!

$$V_i = -1$$

$$V_D = V_i - V$$

$$= -1 - 2$$

$$V_i = -2$$

$$V_D = -2 - 2$$


$$= -4$$

$$V_o = -3 + 2$$

$$= -1$$

$$V_o = -4 + 2$$

$$= -2$$

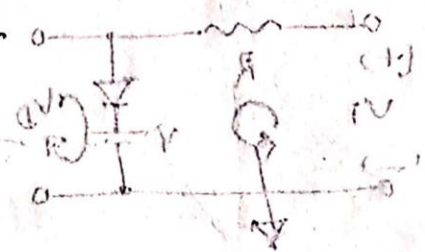

$$-V_i + V + V_D + V = 0$$


$$V_D = V_i - V$$

$$\text{For } V_i = 0 \text{ \& } V = 2$$

$$\text{So } V_D = 0 - 2 = -2$$

$$V_i = 1$$



$$V_D = 1 - 2 = -1$$

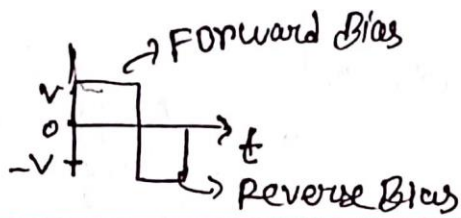

Clipper circuit

→ এটি কাজ শলা Circuit এর একটি অংশ Clipper

Solve:-

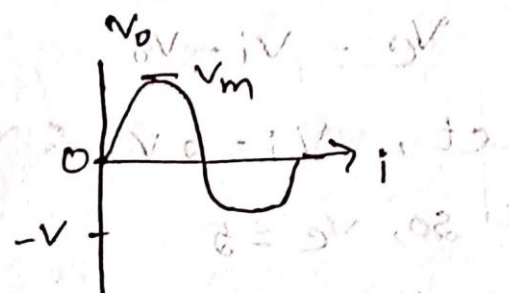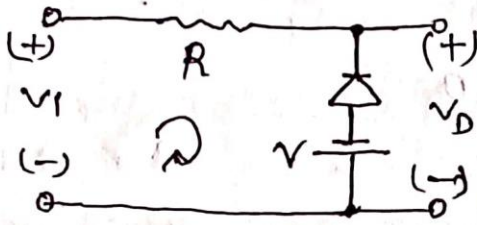

$$-v_i + V_R - V - V_D = 0$$




$$V_D = -v_i - V$$

$$v_o - V_D - V = 0 \implies v_o = V_D + V$$

$$\text{or, } v_o = V_D + V$$

Clamper circuit

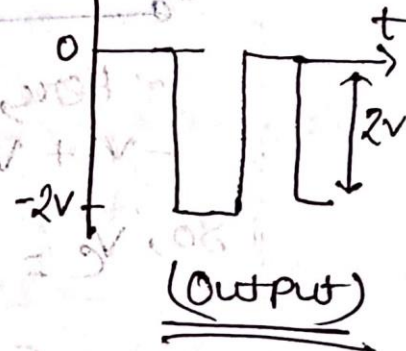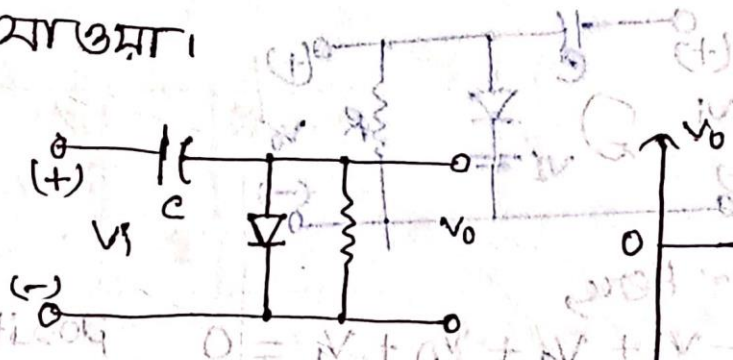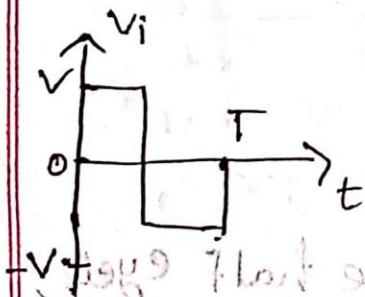এটি কাজ শলা Signal এর একটি Different DC level এ নিয়ে মাওমা।



So, (positive half cycle)

$$-v_i + V_c + v_o = 0$$

positive $\frac{1}{2}$ cycle,

$$V_c = v_i - v_o$$

Let, $v_i = 5V$ & $v_o = 0$

so, $v_c = 5$

Negative $\frac{1}{2}$ cycle,

$$-v_i + v_c + v_o = 0$$


so, $v_o = +v_i - v_c$

Let, $v_i = -5V$,

so, $v_o = -5 - 5$

$= -10V$ (2V का द्विगुण शर होला)

(2) With Biasing voltage

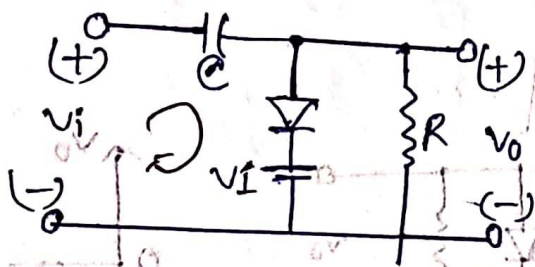

Here,

$$-v_i + v_c + v_D + v_1 = 0$$

positive half cycle

so, $v_c = v_i - v_D - v_1$

$= 5 - 0 - 2$

$= 3V$

so, v_c 3V charge store
शरा

Also,

$$v_D = v_i - v_c - v_1$$

$= v_i - v_1$

Let $v_i = 5V$, $v_1 = 2V$

so, $v_D = 5 - 2 = 3V$

(first way to find out) (other circuit)

Also, $-V_o + V_D + V_1 = 0$

$$-V_o + V_D + V_1 = 0$$

$$\text{So, } V_o = V_D + V_1 = 0 + 2 = 2V$$

Negative half cycle,

Let, $V_i = -5V$

$$V_1 = 2V$$

$$V_D = V_i - V_c - V_1 = -5 - 3 - 2 = -10V$$

So,

$$V_c = V_i - V_D - V_1 = 5 - 0 - 2 = 3V$$


Also,

$$-V_o + V_D + V_1 = 0$$

$$\text{So, } V_o = V_D + V_1$$

$$= -10V + 2$$

$$= -8V$$

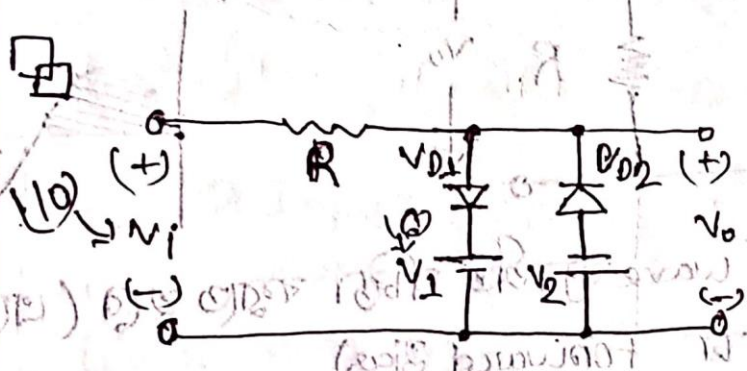

$$-V_i + V_R + V_{D1} + V_1 = 0$$

$$\text{Or, } V_{D1} = V_i - V_1$$

$$= 2 - 6$$

$$= -4 \text{ (Reverse)}$$

$$\text{So, } V_o = V_{D1} + V_1$$


$$= -4 + 6 = 2$$

$$-V_i + V_R - V_{D2} - V_2 = 0$$

$$V_{D2} = -V_i + V_R - V_2$$

$$= -2 - 3 = -5$$

(Reverse)

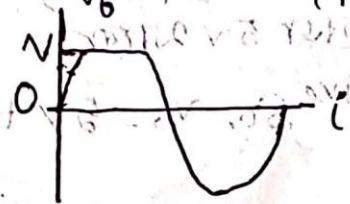





Clipper circuit (School of Engineering)

(Easy way to Remember)

⇒ কোনো Diode এর Anode (+) এর Cathode (-) হল তা Forward Bias হবে।

Anode এর wave থাকলে তাই হবে output.

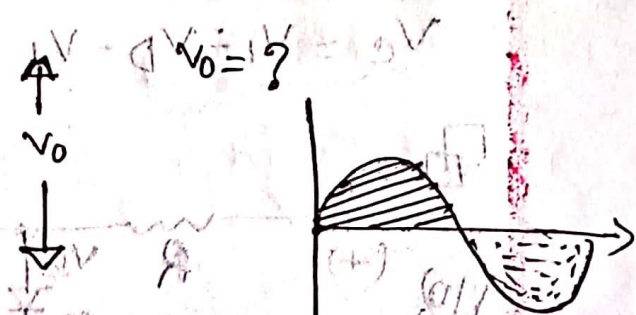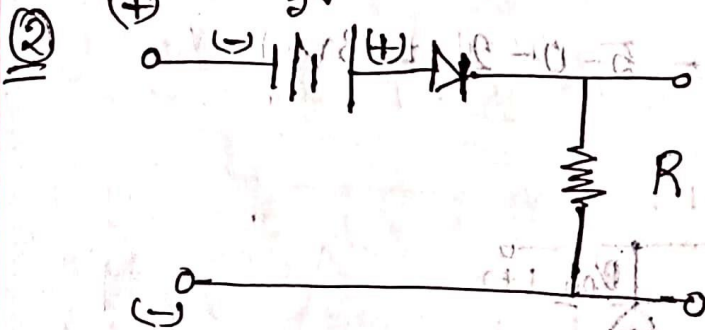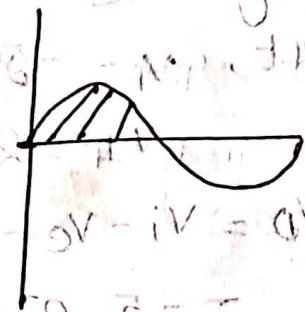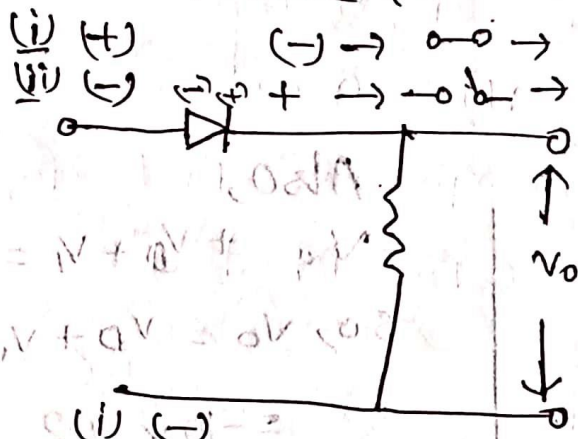
(i) (+) (-) → o-o → close switch এ output ফালায়।
 (ii) (-) (+) → o-o → Open switch → এর ফলে এর কোনো output হবে না।



সমাধান - ১) প্রথমে wave ব্যাখ্যা চিন্তা করতে হবে (এক্ষেত্রে Diode এর Forward Bias)

Output -

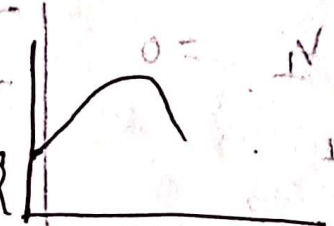০. ২০ অক্ষর
 ২০ নি লার্ড Battery
 ছাড়া ৫V থাকে



Positive So, $V_o = 5V + 20V = 25V$

১) Negative: $\left[\begin{array}{|c|} \hline + \\ \hline \end{array} \right] \left[\begin{array}{|c|} \hline - \\ \hline \end{array} \right] \left[\begin{array}{|c|} \hline + \\ \hline \end{array} \right]$ (৪)

২) $20V$ and $+5V$ (৫)

$$= -15V$$


৩) $5V$ output (৬)

৪) $5V$ and $+5V$ (৭)

৫) $5V$ (৮)

৬) $5V$ (৯)


Clamper circuit

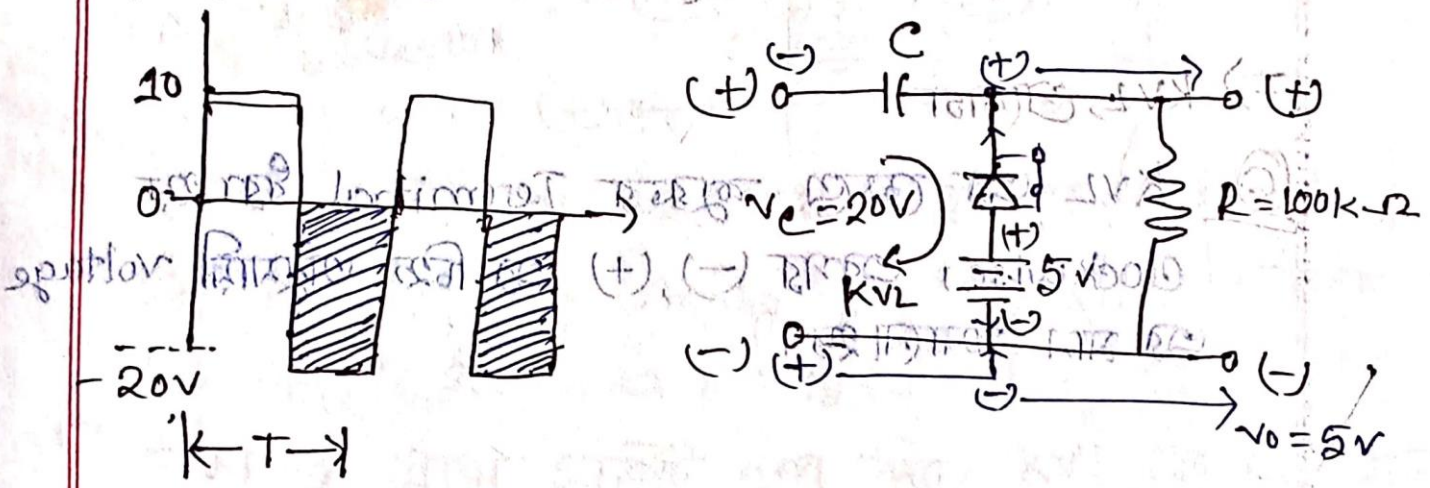

কর্ত:- ১) Input এ কোন cycle দিলে Diode Forward Bias।

- ২) উচ্চ চিহ্ন উপরে (-) দিলে এবং নিচে (+) দিলে Forward Bias)
- ৩) ক্ষুদ্রতম (এই চিহ্ন) Negative দিলে ক্ষুদ্র হবে
- ৪) এখানে Diode এর ডিফারেন্স দিলে (-) এম Output এ (-) হবে এবং (+) এম Output এ positive হবে।

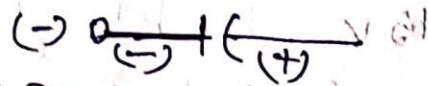
৪) আবার Capacitor এর (+), (-) নির্ধারণ করতে হবে।
 ক্ষুদ্রতম বা সর্বনিম্ন ভোল্টেজের পুরাতন এক দাঁড়ান হবে। অপর



যে Condition দ্বারা solve করা হচ্ছে।
 এখানে এই Capacitor এ voltage drop হবে (V_c)।
 এর নির্ণয় করতে হবে KVL রূপ চালাতে হয়।

⇒ KVL প্রমাণ।

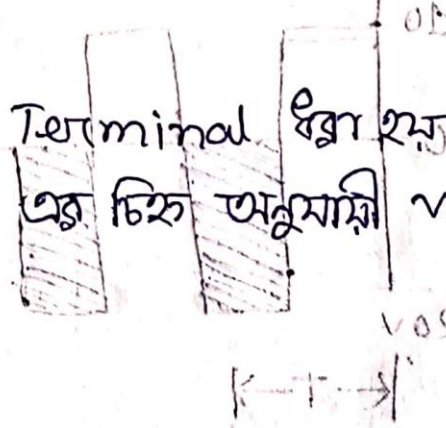৬) KVL এর ক্ষেত্রে ক্ষুদ্রতম Terminal ধরা হয়
 clockwise, অপর (-), (+) এর চিহ্ন অনুযায়ী voltage
 এর মান বমানো হয়।



বর্তমানের ক্ষেত্রে ক্ষুদ্রতম বা সর্বনিম্ন ভোল্টেজের পুরাতন এক দাঁড়ান হবে। অপর
 ক্ষুদ্রতম বা সর্বনিম্ন ভোল্টেজের পুরাতন এক দাঁড়ান হবে। অপর
 ক্ষুদ্রতম বা সর্বনিম্ন ভোল্টেজের পুরাতন এক দাঁড়ান হবে। অপর
 ক্ষুদ্রতম বা সর্বনিম্ন ভোল্টেজের পুরাতন এক দাঁড়ান হবে। অপর


অধিকারী ব্যক্তিগণের সম্মুখে
 এই প্রকল্পটি ১৯৯০ সালে মন্ত্রণালয়ের অধীনে
 এই অধিকারী ব্যক্তিগণের সম্মুখে অধিকারী ব্যক্তিগণের সম্মুখে

=> Solve :- Capacitor এর Charging volt.

KVL প্রয়োগ করতে পারি,

$$+20 - V_c + 5V = 0$$

So, $V_c = 25V$

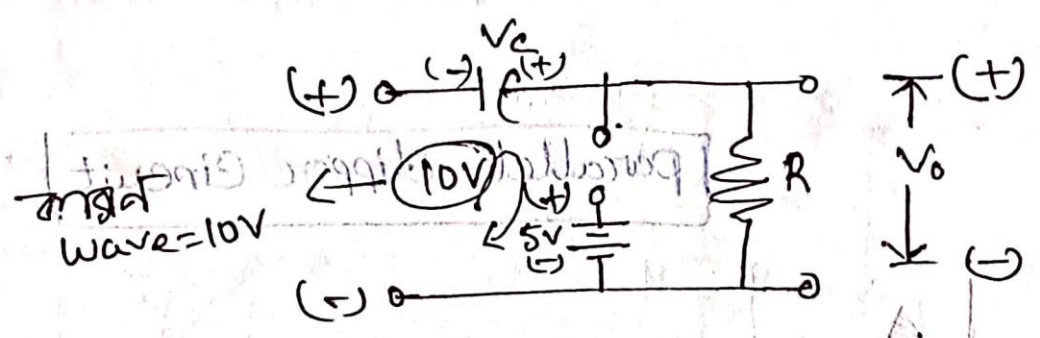

এখানে, যদি positive দেওয়া হয় তাহলে Cathode
 হয় positive আর Anode হয় Negative। ফলে
 এটি open switch এ পরিণত হয়। এর ফলে
 আমাদের পুরো সার্কিট খুঁপ দিয়ে KVL প্রয়োগ করতে
 হবে। (কারণ open switch output পাওয়া যায় না।)

=> So, KVL প্রয়োগ করতে পারি,

$$-10V - V_c + V_o = 0$$

So, $-10V - 25 + V_o = 0$

অর্থাৎ, $-35V = -V_o$

So, $V_o = 35V$






So, Positive = 35V
 Negative = 5V



P.T.O

Diode ଏବଂ କ୍ୟାପାସିଟର Negative

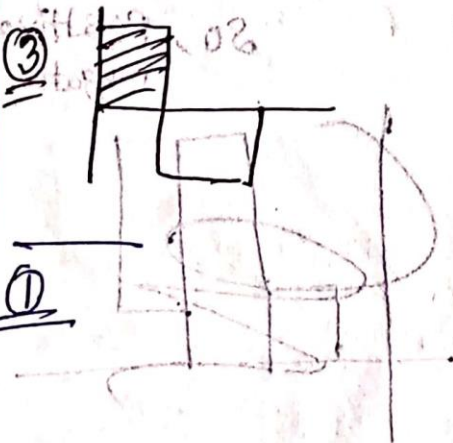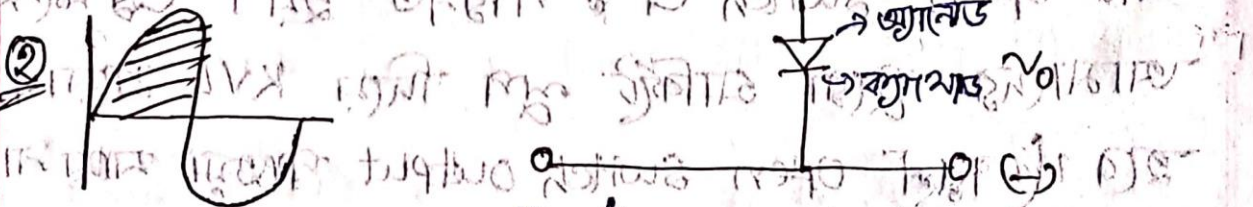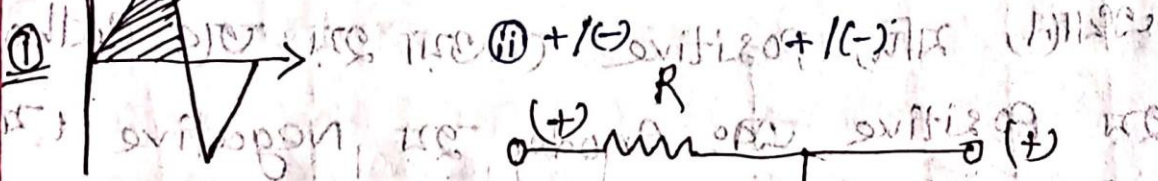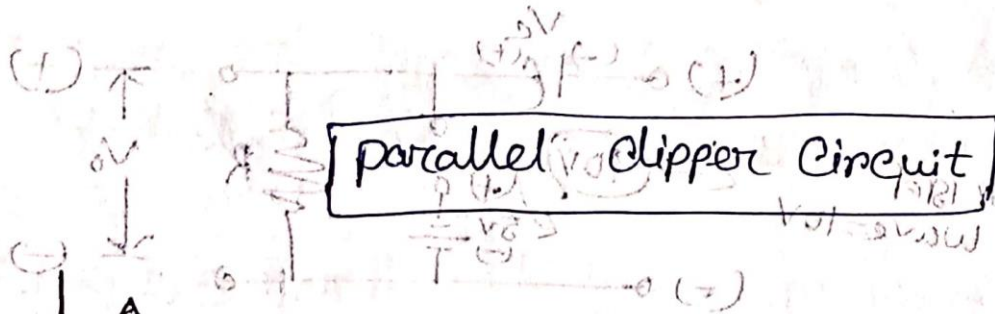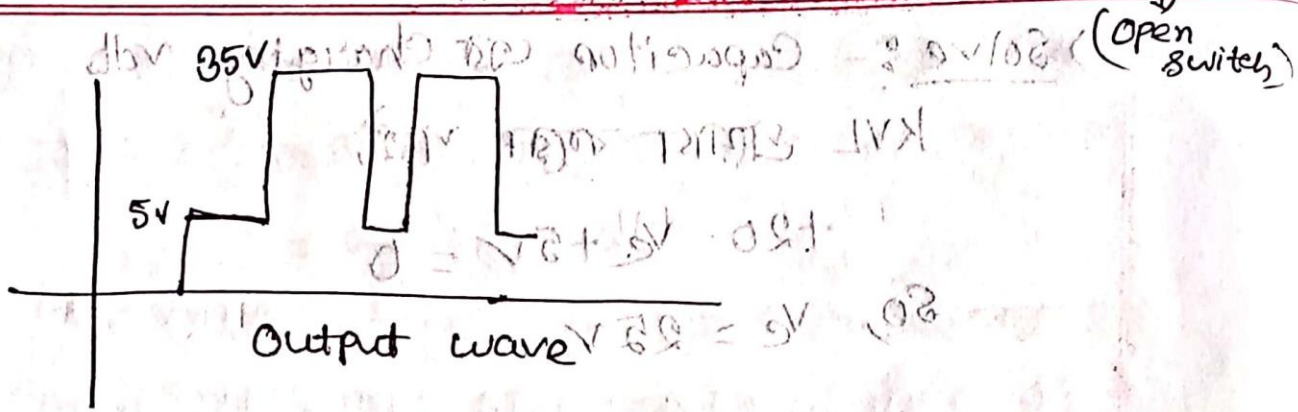Anode ଏ positive ହଲେ Diode ଅଫ Forward Bias
 କାଥୋଡ୍, Cathode ଏ positive ଏବଂ Anode ଏ Negative ଅଫ Reverse bias




$$0 = 0V - V - V_{01} -$$

$$0 = 0V + 3V - V_{01} -$$

$$0V = 3V - V_{01}$$



$$V_{01} = 3V$$

2 Output

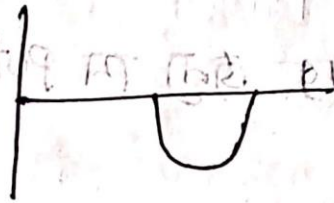


[কারণ Forward Bias এ OFF switch হওয়ায় electron মুঠে এর তির দিয়ে চলে যায়, Reverse Bias এ পাঠে না।]

math

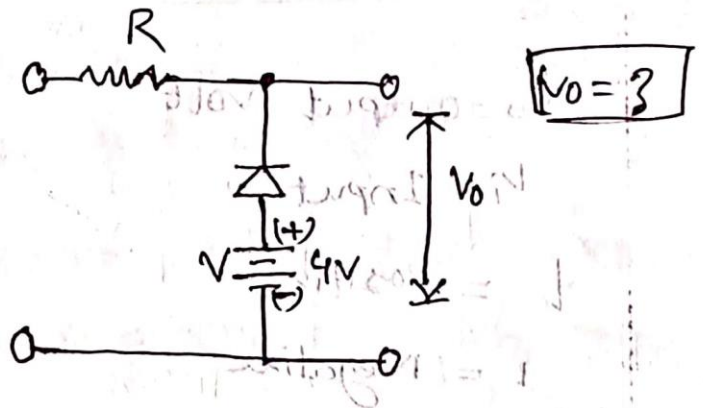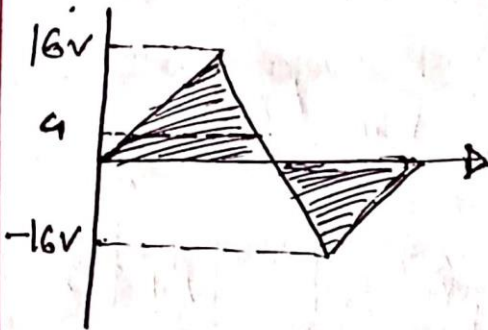

Output:-

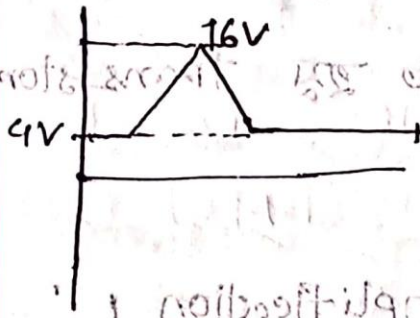


(i) Battery wave এবং Signal wave বকনমু।

সিলিকন Diode:-

$\Delta i = 0.7v$ drop হবে। সেক্ষেত্রে Battery তে মত

volt থাকবে তার থেকে মাইনাস হবে।

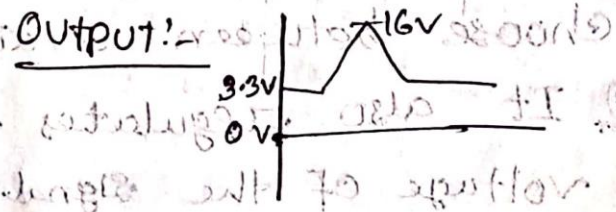

~~transistor~~

Barrier Potential:-


P region n
n " P to সাওয়ায় ক্রম potential
এর সৃষ্টি হয়।

$V_o =$ output volt

$V_i =$ Input "

L = positive

I = Negative

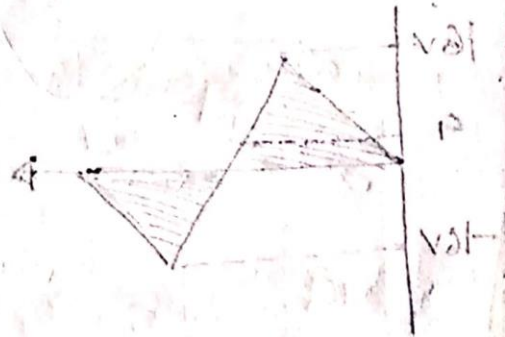

Transistor

এটি দুই ধরনের নিম্ন গাঠিত হয় transistor,

P-N-P, N-P-N।

Transistor এর মূল কাজ Amplification।

Amplification means increasing the signal strength.

⊗ A transistor also acts as a switch to choose between available options.

⊗ It also regulates the incoming current & voltage of the signal.

Construction:-

N-P-N



OR

P-N-P

⇒ The transistor is a three terminal solidstate device which is formed by connecting two diodes back to back. Hence it has got two PN junctions.

⇒ This type of connection offers two types of transistors. They are PNP & NPN which means an N-type material between two p types and the other is a p-type material between two N-type respectively.

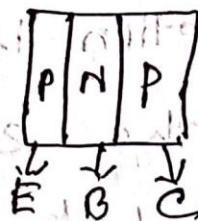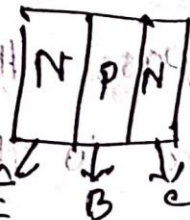• The ~~the~~ three terminals drawn from the transistor indicate Emitter, Base & Collector terminals.



⇒ Construction OF PNP & NPN Transistors

Emitter:-

- The left hand side of the shown structure can be understood as Emitter.
- This has a moderate size and is heavily doped as its main function is to supply a number of majority carriers, either electrons or holes.
- As this emits majority carriers, it is called as an Emitter.
- This is simply indicated with the letter E.

Base:-

- The middle material in the above figure is the Base.
- This is thin & lightly doped.
- Its main function is to pass the majority carriers from the emitter to the collector.
- This is indicated by the letter B.

Collector :-

- The right-side material in the above figure can be understood as a collector.
- Its name implies its function of collecting the carriers.
- This is a bit larger in size than

emitter and base. It is moderately doped.


- This is indicated by the letter c.

Symbol :-


Symbol :-

- The arrow-head in the figures indicated are the emitter of a transistor.
- Due to the specific functions of emitter & collector, they are not interchangeable. Hence the terminals are always to be kept in mind while using a transistor.
- In a practical transistor, there is a notch

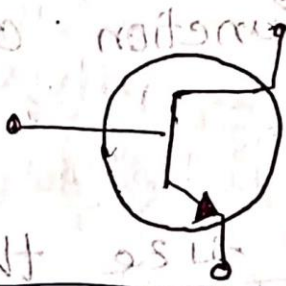present near the emitter lead for identification. The PNP & NPN transistors can also be differentiated using a Multimeter.




Symbol of NPN transistor

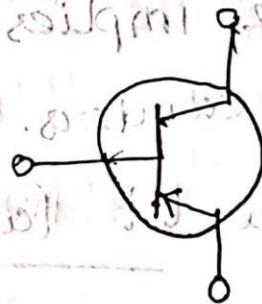

Symbol of PNP transistor

Transistor Biasing:-

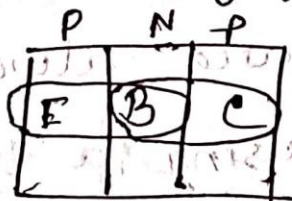As we know that a transistor is a combination of two diodes, we have two junctions here. As one junction is between the emitter & base, that is called as Emitter-Base junction & likewise, the other is collector-base junction.



• (Biasing is controlling the operation of the circuit by providing power supply.) The

Function of both the PN junctions is controlled by providing bias to the circuit through some DC supply.


⊗ Emitter-Base junction के अन्दर Forward Bias रहेगा।

⊗ Collector-Base junction के अन्दर Reverse Bias रहेगा।

• In p-n-p junction,

⊗ The N-type material is provided negative supply & P-type material is given positive supply to make the circuit Forward bias.

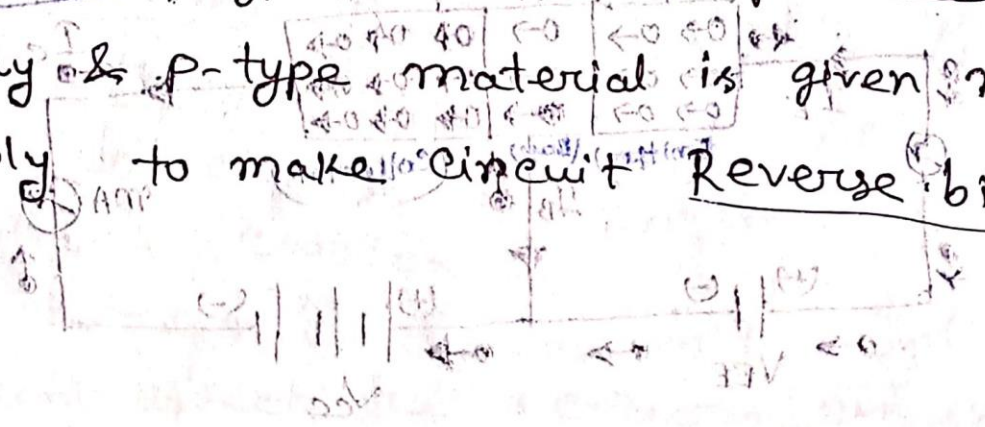⊗ The N-type material is provided positive supply & P-type material is given negative supply to make circuit Reverse bias.




⊕ By Applying the power, the emitter-Base junction is always forward biased as the emitter resistance is very small. The collector base junction is reverse biased, and its resistance is a bit higher. Therefore, it is called Transistor [Transfer of Resistance].

✗ Conventional current:-

The direction of current indicated in the circuits above, also called as the conventional current, is the movement of hole current which is opposite to the electron current.

Operation of PNP Transistor

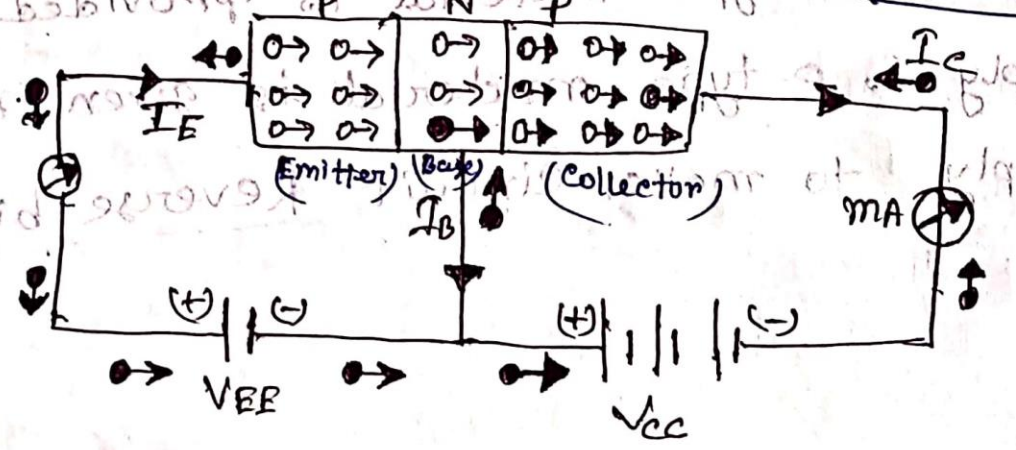

- The voltage V_{EE} provides a positive potential at the emitter which sweeps the holes in the p-type material & these holes cross emitter-base junction, to reach the base region.
- There a very low percent of holes recombine with free electrons of N-region. This provides very low current which constitutes the base current I_B .
- The remaining holes cross the collector-base junction, to constitute collector current I_C , which is the hole current.

Hence, we can understand that,


- The conduction in PNP transistor takes place through holes.
- The collector is slightly less than the emitter current.
- The increase or decrease in the emitter current affects the collector current.

- The voltage V_{EE} provides a positive potential at the emitter which repels the holes in the p-type material & these holes cross emitter-base junction, to reach the base region.
- There a very low percent of holes recombine with free electrons of N-region. This provides very low current which constitutes the base current I_B .
- The remaining holes cross the collector-base junction, to constitute collector current I_C , which is the hole current.

Hence, we can understand that,

- The conduction in PNP transistor takes place through holes.
- The collector is slightly less than the emitter current.
- The increase or decrease in the emitter current affects the collector current.

Operation of NPN Transistor

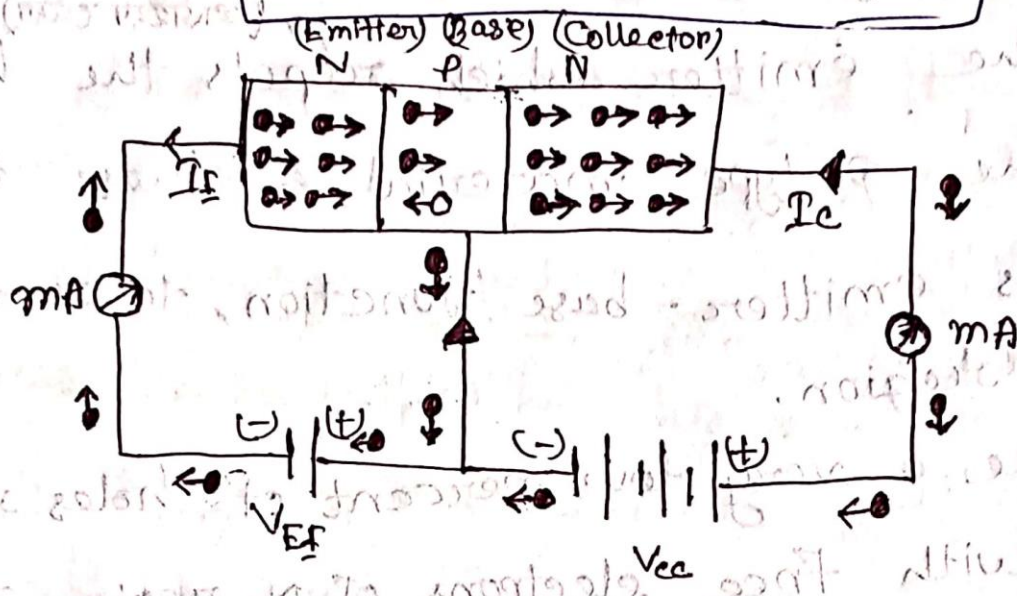

⇒ The voltage V_{BE} provides a negative potential at the emitter which repels the electrons in the N-type material and these electrons cross the emitter-base junction, to reach the base region.

⇒ There a very low percent of electrons recombine with free holes of p-region. This provides very low current the base current I_B .

⇒ The remaining electrons cross the collector-base junction, to constitute the collector current I_C .

Hence we can understand that -

- (i) The conduction in a NPN transistor takes place through electrons.
- (ii) The collector current is ~~higher~~ higher than the emitter current.
- (iii) The increase or decrease in the emitter current affects the collector current.

Advantages of Transistor

- 1] High voltage gain.
- 2] Lower supply voltage is sufficient.
- 3] Most suitable for low power applications.
- 4] Smaller & lighter in weight.
- 5] Mechanically stronger than vacuum tubes.
- 6] NO external heating required like vacuum tubes.
- 7] very suitable to integrate with resistors & diodes to produce ICs.

$$\beta_{AC} = \frac{I_C}{I_B} = \frac{I_C}{I_B} = \frac{I_C}{I_B} = \frac{I_C}{I_B}$$


$$\frac{I_C}{I_B} = \frac{I_C}{I_B} = \frac{I_C}{I_B} = \frac{I_C}{I_B}$$

Configurations of Transistor

Transistor has 3 terminals. The emitter, the base & the collector. Using these 3 terminals the transistor can be connected in a circuit with one terminal common to both input & output in a three different possible configurations.

The three types of configurations are Common Base, Common Emitter, Common Collector configurations. In every configuration the emitter junction is forward biased & the collector junction is reverse biased.

Common-Base Configuration:-

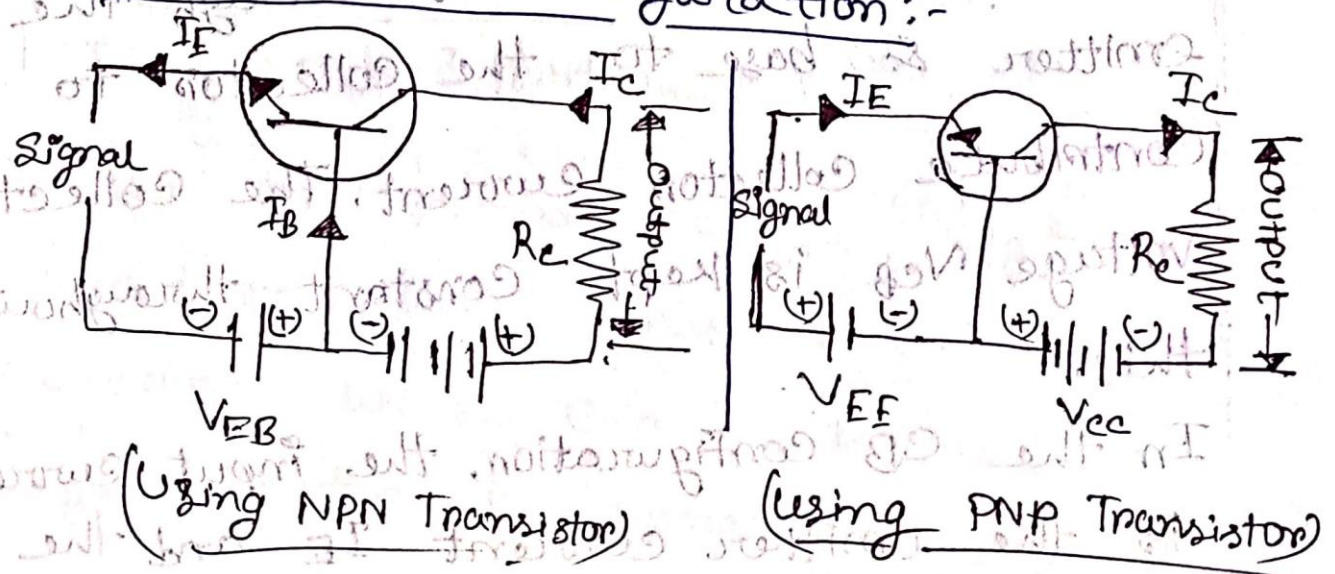

$$\frac{\text{Output}}{\text{Input}} > 1 = \text{Amplification}$$

$$\Rightarrow \frac{V_o}{V_i} \Rightarrow \frac{I_o}{I_i} \Rightarrow \frac{P_o}{P_i} \Rightarrow \frac{I_c}{I_E}$$

$$I_E (\text{emitter current}) = I_B + I_C$$

$I_C < I_E$. That means $\frac{I_C}{I_E} < 1$

⇒ Common Base Configuration এর ক্ষেত্রে Current এর কোনো Amplification সম্ভব না।

এর মানে হলো ~~Current~~ Common Base Configuration এর ক্ষেত্রে কোনো Amplification সম্ভব না।

⇒ In NPN transistor in CB configuration, when the emitter voltage is applied, as it is forward biased, the electrons from the negative terminal repel the emitter electrons & current flows through the emitter & base to the collector to

contribute collector current. The collector voltage V_{CB} is kept constant throughout this.

In the CB configuration, the input current is the emitter current I_E and the

Output current is the collector current I_c .

Current Amplification Factor α :-

The ratio of change in collector current ΔI_c to the change in emitter current ΔI_E when the variation of change in collector current ΔI_c to the change in emitter current ΔI_E when collector voltage V_{CB} is kept constant, is called as current amplification factor. It is denoted by α

$$\alpha = \frac{\Delta I_c}{\Delta I_E} \text{ at constant } V_{CB}$$

Total collector current:-

$$I_c = \alpha I_E + I_{cbo} \text{ leakage}$$

If the emitter-base voltage $V_{EB} = 0$, even then, there flows a small leakage current, which can be termed as I_{cbo} collector-base current without open

The collector current therefore can be expressed as

$$I_c = \alpha I_E + I_{CBO}$$

we know,

$$I_E = I_C + I_B \quad \text{--- (1)}$$

$$I_C = \alpha (I_C + I_B) + I_{CBO} \quad \text{--- (2)}$$

$$I_C (1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \left(\frac{\alpha}{1 - \alpha} \right) I_B + \left(\frac{I_{CBO}}{1 - \alpha} \right)$$

$$I_C = \left(\frac{\alpha}{1 - \alpha} \right) I_B + \left(\frac{1}{1 - \alpha} \right) I_{CBO}$$

Common Emitter (CE) Configuration


PNP → Forward Bias হলে $p(+)$ ও $n(-)$

(-) এর সঙ্গে যুক্ত রাখতে হবে, $V_{EB} = 0$

$V_{EB} = 0$ If the emitter-base voltage

even then there flows a small current which can be termed as collector-emitter current

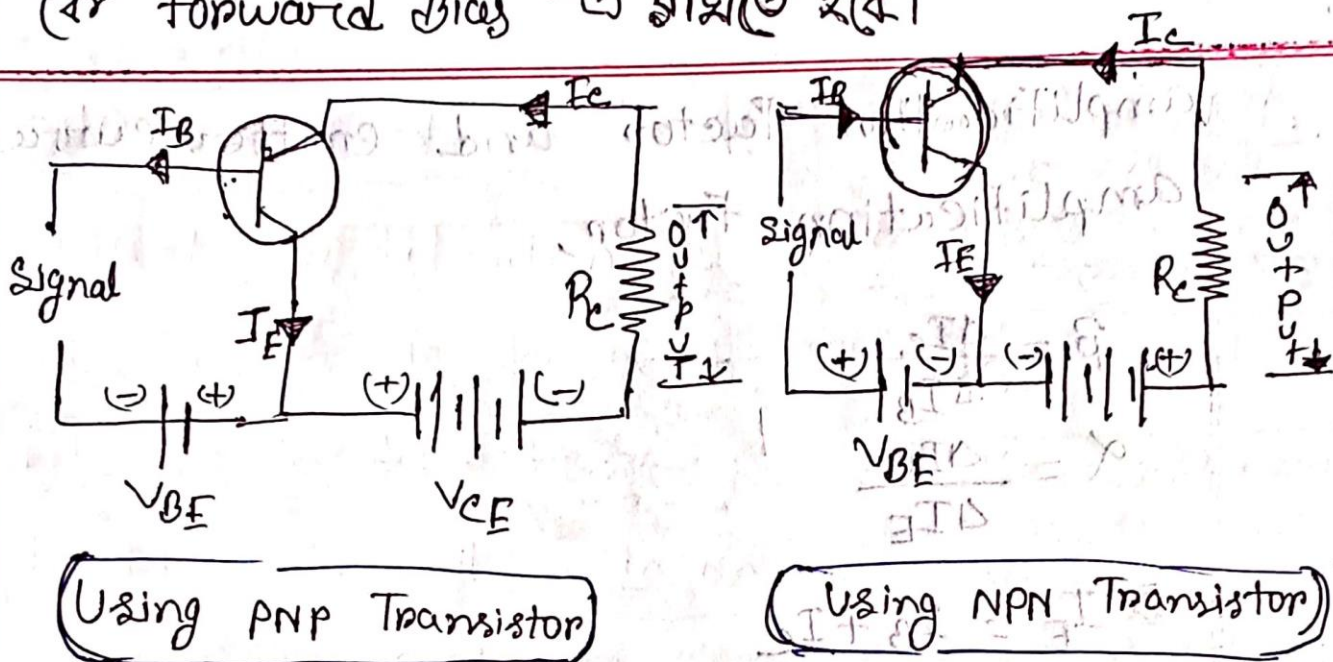ଏହା ଏକ Configuration ଯେ କିଏ Emitter
 ଥିବା Forward Bias ଏ ଗ୍ରହଣ କରେ ।



⇒ The emitter junction is forward bias & collector junction is reversed biased. The flow of electrons is controlled in the same manner. The input current is the base current I_B and the output current is the collector current I_C here.

Base current Amplification Factor (β)

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Relation between β & α :-


Let us derive the relation between base current

Amplification Factor and emitter current

Amplification Factor

$$\beta = \frac{\Delta I_c}{\Delta I_b}$$
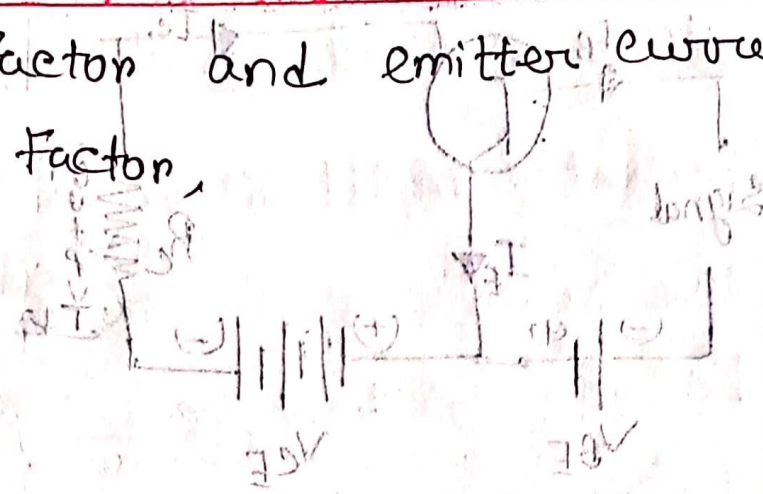
$$\alpha = \frac{\Delta I_c}{\Delta I_E}$$



$$I_E = I_B + I_C$$

$$I_E = I_B + I_C$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

~~$I_C = \beta I_B + I_{C0}$~~

Relation between β & α :-

Let us derive the relation between base

Fixed-Biased Circuit (কোনো উদাহরণ) :-

Emitter Terminal এ কোনো Resistance লাগানো
শক্ত নেই।

Fixed-Bias Circuit :-

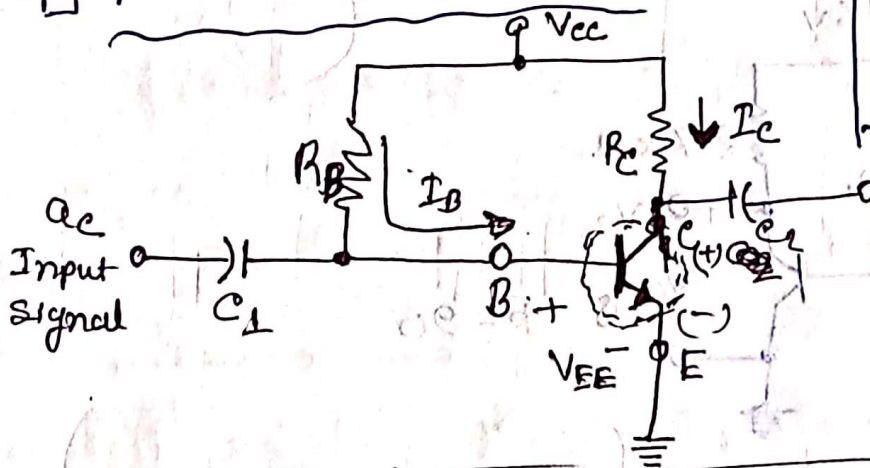


Figure:- Fixed-Bias Circuit

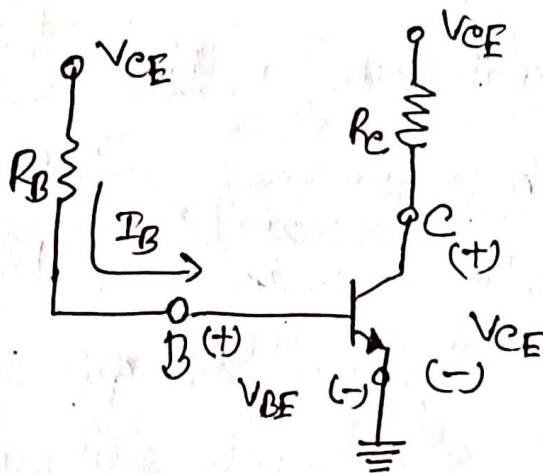


Figure:- equivalent of

একটি AC signal কে Ignore করে ফেলে Fixed-Bias Circuit ও হিসেব করা যায়।

এই একটি অংশ Base terminal এর মধ্যে, আরেকটি মুক্ত করা হয় Resistance এর মাধ্যমে এক বলা হয় Base Resistance আরেকটি terminal এর Resistance দেওয়া হয়। collector Terminal এর মধ্যে মুক্ত করা হয়। একে বলা collector Resistance


Solve!

প্রথম I_B বের করা (Base terminal Flow current)

$\Rightarrow I_B$ বের করার জন্য Input side side মান ব্যবহার করা হবে।

$\Rightarrow V_C$ বের করার জন্য Output side এর মান ব্যবহার করা হবে।

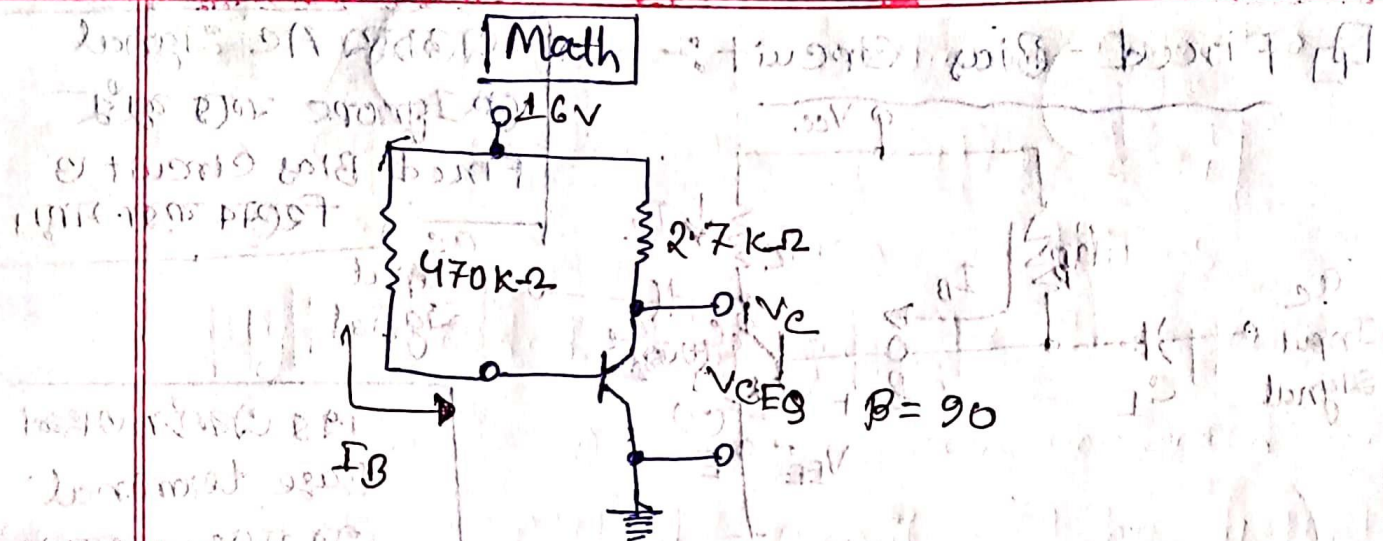Fixed Bias Circuit (Common Emitter) - Example 1



Determine :-

- (i) I_B
- (ii) I_C
- (iii) V_{CE}
- (iv) V_{BE}

$V_{BE} = V_B - V_E = V_B - 0$
 $= V_B = 0.7V$

Steps

- 1. প্রথম কাজ হলো I_B বের করা।
- 2. এরপর $I_C = \beta I_B$ বের করা।
- 3. V_{CE} বের করা I_C হতে।

Base Emitter \rightarrow Forward Bias এ থাকবে।

Collector Base \rightarrow Reverse Bias এ থাকবে।

All Formulas

$$V_{CE} + I_{E}R_E - V_{CC} = 0$$

$$\text{or, } V_{CE} = V_{CC} - I_{E}R_E \quad \text{--- (1)}$$

সকসময়,

$$\boxed{V_E = 0}$$

$$\boxed{V_{CE} = V_C - V_E} \quad \text{--- (2)}$$

$$\boxed{V_{CE} = V_C} \quad \text{--- (3)}$$

$$\boxed{V_{BE} = V_B - V_E} \quad \text{--- (4)}$$

$$\boxed{V_{BE} = V_B} \quad \text{--- (5)}$$

Transistor Saturation

The term saturation is applied to any system where levels have reached their maximum values. A saturated sponge is one that cannot hold another drop of liquid. For a transistor operating in the saturation region. The current is a maximum value for the particular design. Change the design & the corresponding saturation level may rise or drop. Of course, the highest saturation level

is defined by the maximum collector current as provided by the specific sheet.

⚡ Saturation conditions are normally avoided because the base-collector junction is no longer reverse-biased and the output amplified signal will be distorted.

$$V_{CE} = V_{CC} - I_C R_C$$

we call it saturation when,

$V_{CE} \leq 0.3V$ [অর্থাৎ এই সময়ে transistor টা saturation region এ প্রবেশ করে]

$$V_{CB} = V_{CE} - V_{BE}$$

সতর্কতায়, $V_C - V_B$ > মান (+) হতে হবে।

V_{CE} কে 0 ধরে মোড করা হয়, কারণ 0.3 এর 0 এর মাঝে যেমন কোনো পার্থক্য নেই।

Transistor Biasing:

Transistor Biasing का दूहेर उलयः

(i) TO set an operating point.

(ii) TO ensure temperature stability.

☐ We know that,

$$I_c = \beta I_B + I_{CEO}$$

Fixed

☐ Load-Line Analysis :-

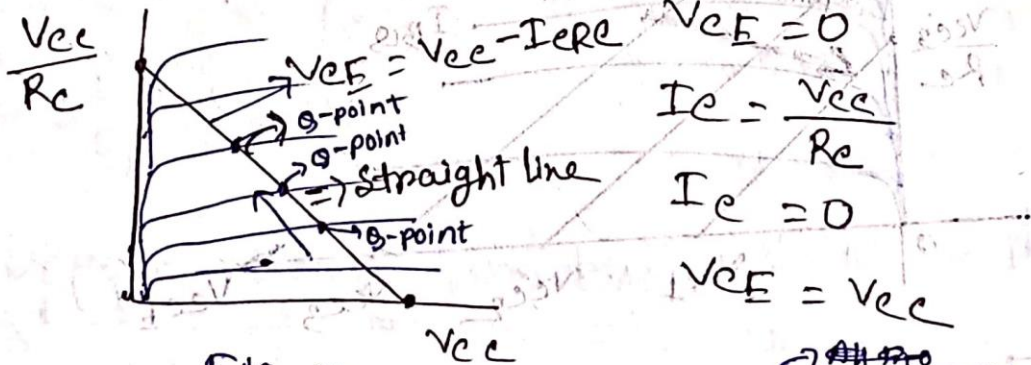


Fig: Movement of Q-point with increasing levels of I_B


$V_{CE} = V_{CC} - I_c R_c$ is similar to a straight line

eqn

$$y = mx + c$$

or, $V_{CE} = R_c I_c + V_{CC}$

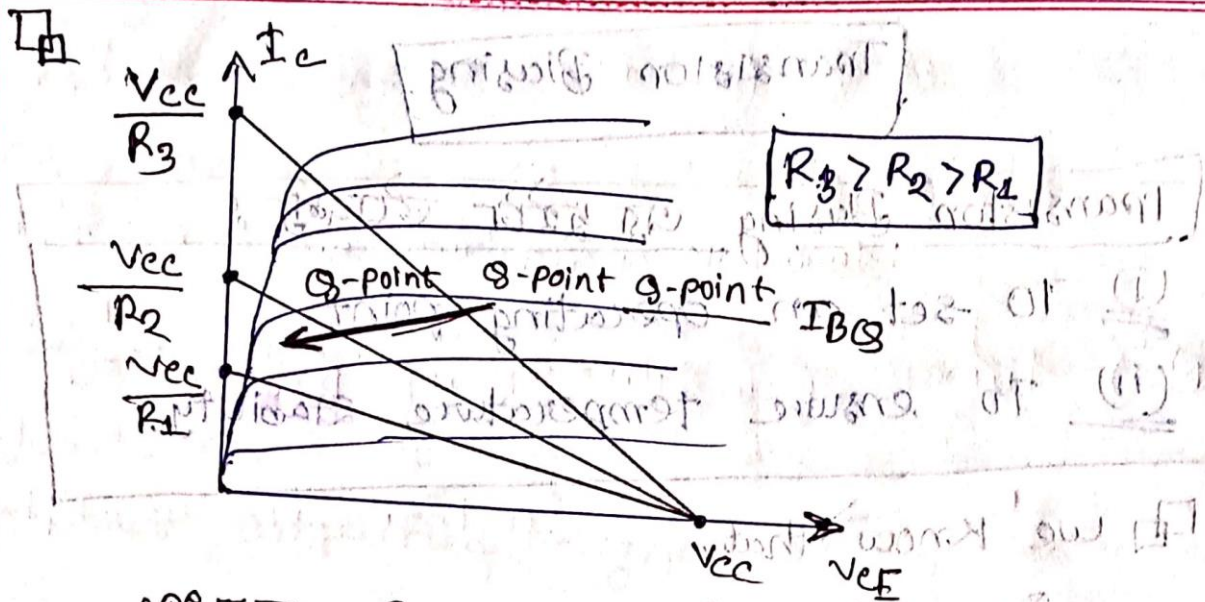⊛ The straight line in the figure is known as Load-Line.



এখানে R_c বাড়ানো-কমানোর মাধ্যমে
 operating point ~~load line~~ এর চ্যাবির্ভন করা সম্ভব।

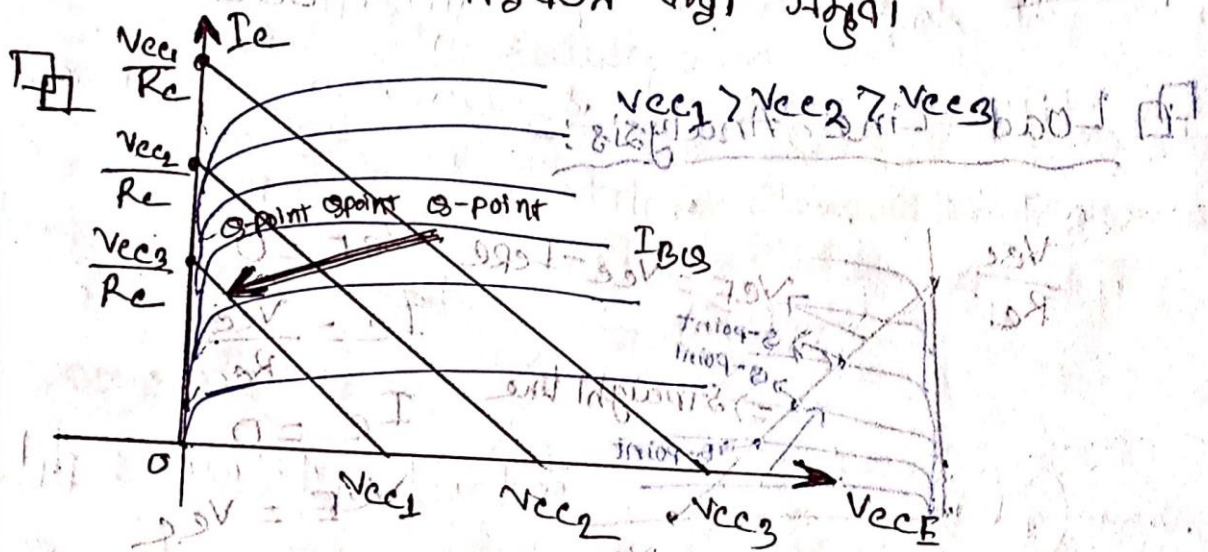


Figure: Effect of lower values of V_{cc}
 on the load line & Q-point

এখানে V_{cc} এর মান বাড়ানো-কমানোর মাধ্যমে
 operating point এর চ্যাবির্ভন হয়।

Fixed Bias Design

V_{BE} দিগ Reverse Bias test ২৫

Fixed Bias এর ডিজাইনিং এর ক্ষেত্রে,
 V_{CC} , R_B ও R_C এর বন্টন হয়

Emitter-Stabilized Bias Circuit:-

Note:-

(i) $V_{AB} = V_A - V_B$ [অর্থাৎ, V_A point V_B point-এর শক্ত। কি পজিটাইভ potential এ আছে]

(ii) $V_A = V_A - V_0$ [অর্থাৎ, V_A point Ground potential-এর শক্ত। কি অক্সিমাম আছে।]

Emitter Bias Circuit এর ক্ষেত্রে stability বৃদ্ধি পাওয়া যায়।

4.5] Voltage Divider Bias Circuit:-

4.6] DC BIAS with Voltage Feedback:-

4.7] Miscellaneous Bias Configuration:-

(page-174)

* Biasing Circuit:-

Transistor Switching Network:-

ট্রানজিস্টর দিয়ে Switching circuit তৈরি।

Bias Stabilization:-

The stability of a system is a measure of the sensitivity of a network to variations in its parameters. In any amplifier employing a transistor the collector current I_c is sensitive to each of the following parameters.

Stability Factors, $S(I_{co})$, $S(V_{BE})$ and $S(\beta)$:-

$S(I_{co}) = \frac{\Delta I_c}{\Delta I_{co}}$ — (1) → Reverse saturation current

$S(V_{BE}) = \frac{\Delta I_c}{\Delta V_{BE}}$ — (2) → Base-Emitter voltage

$S(\beta) = \frac{\Delta I_c}{\Delta \beta}$ — (3) → Current Amplification Factor

IF its output is under control then it's system is stable

কোনটা I_c এর মান চলেবে?

The higher the stability factor, the more sensitive the network to variations in that parameter.

$S(I_{co})$:- [Emitter Bias Configuration]

$$S(I_{co}) = (\beta + 1) \cdot \frac{1 + R_B/R_E}{(\beta + 1) + R_B/R_E} \quad (4.54)$$

For $(R_B/R_E) \gg (\beta + 1)$ will reduce to the following

$$S(I_{co}) = \beta + 1 \quad (4.55)$$

Feedback - Bias configuration → (কিসক দায়ের স্থানীয় লিখা আছে)

Physical Impact:-

$$\text{Equation } \left(I_B = \frac{V_{CC} - V_{BE}}{R_B} \right)$$

[Equations of the type developed above often fail to provide a physical sense for why the networks perform as they do]

with the collector current determined by,

$$I_C = \beta I_B + (\beta + 1) I_{co} \quad (4.61)$$

R_B হতে R_E এর
 মাত্র বাড়লে স্টাবিলিটি
 তাই সোপান হবে।

Field Effect Transistors (FET)

⊛ BJT ও FETঃ (সামঞ্জ)

BJT :- এটি একটি Current Control Device.

FET :- এটি একটি voltage Control Device.

⊛ BJT transistor is a bipolar device, কারণ hole ও electron উভয়ই Current Conduction অংশগ্রহণ করে।

FET is a unipolar device depending solely on either electron (n-channel) or hole (p-channel) conduction.

⊛ FET is high input impedance. At level of 1 to several hundred megohms, it far exceeds the typical input resistance levels of the BJT transistor configurations. A very important characteristic in the design of


⊛ FET খুব ছোট করে বানাতে যায়। এটাকে Integrated Circuit (IC) হিসেবে তৈরি করা যায়।

There are two types OF FETs ~~will be~~ introduced in this chapter.

1) The Junction Field-Effect Transistor (JFET)

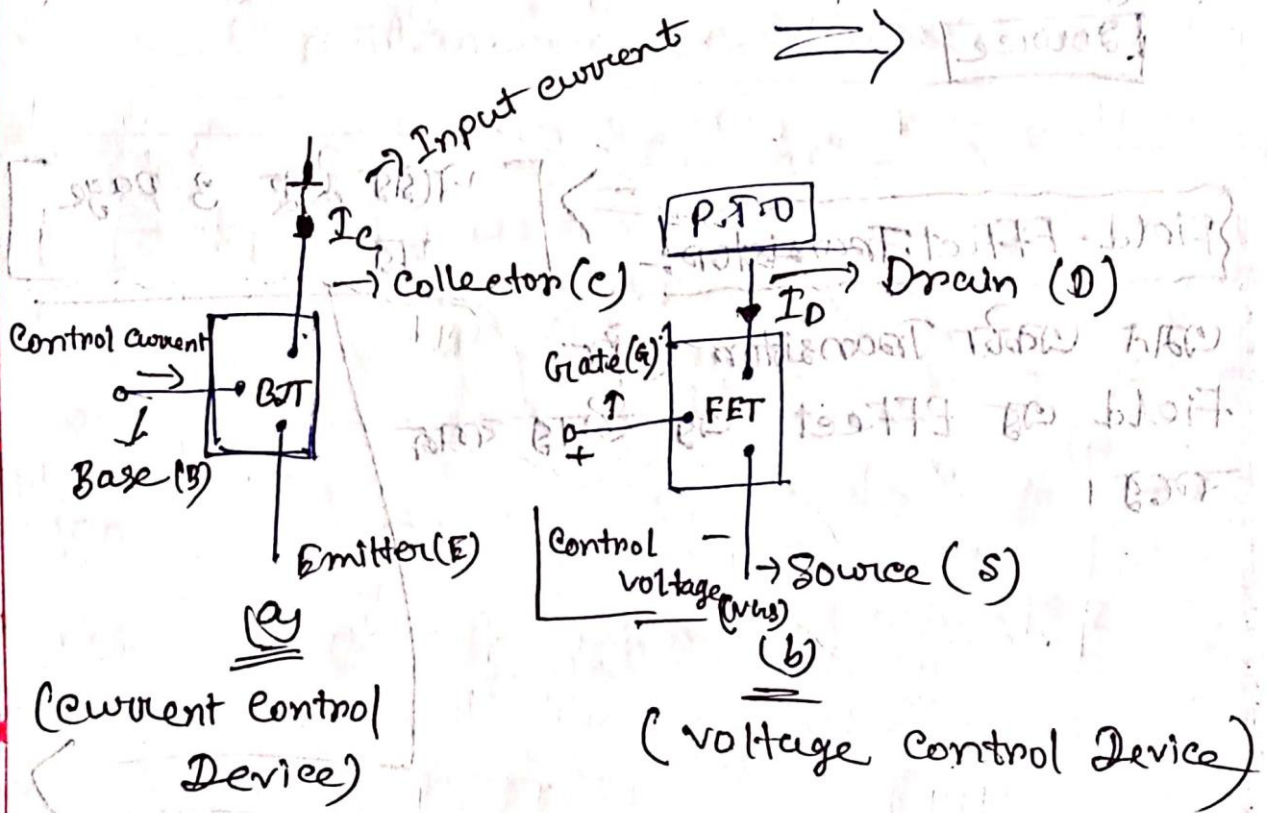2) The Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET).

The MOSFET category is further broken down into depletion and enhancement types.





④ FET:-

Amitter ——— Source


Base ——— Gate

Collector ——— Drain

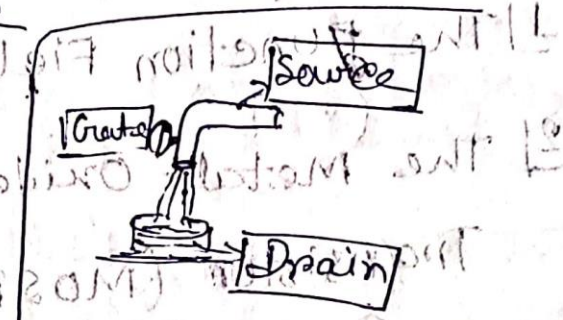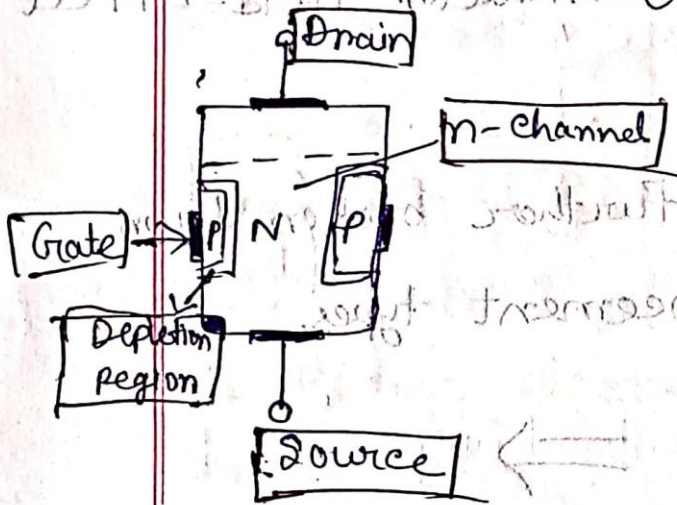

Field-Effect Transistor ⇒ [চারটি পৃষ্ঠ 3 page]
চার

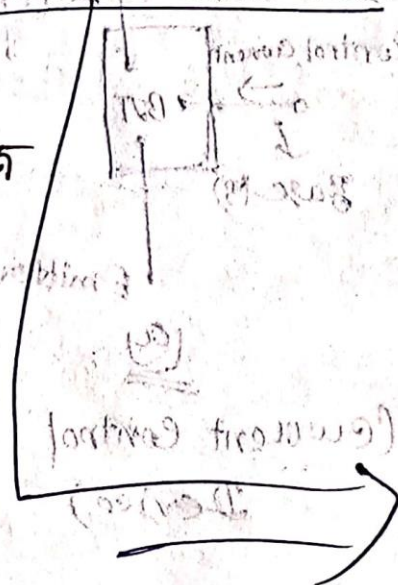এমন একটা Transistor যেটা
 Field এর Effect এর উদ্বৃত্ত কাজ
 করে।



Chapter - 5

Field Effect Transistors.

ad

4.12] Bias Stabilization:-

The stability of a system is a measure of the sensitivity of a network to variations in its parameters.

In any amplifier employing a transistor the collector current I_c is sensitive to each of the following parameters.

Variation of Silicon Transistor parameters with Temperature

$T(^{\circ}C)$	$I_{CO} (nA)$	β	$V_{BE} (V)$
-65	0.2×10^{-3}	20	0.85
25	0.1	50	0.65
100	20	80	0.48
175	3.3×10^3	120	0.3

Operating point & Temperature এর সাথে পরিবর্তন

২৫।

Stability Factors, $S(I_{CQ})$, $S(V_{BE})$, and $S(\beta)$:-

$$S(I_{CQ}) = \frac{\Delta I_C}{\Delta I_{CQ}} \quad (4.51)$$

$$S(V_{BE}) = \frac{\Delta I_C}{\Delta V_{BE}} \quad (4.52)$$

$$S(\beta) = \frac{\Delta I_C}{\Delta \beta} \quad (4.53)$$

[Stability Factor को मान मूल्य कम करते रहे]

Note 2

For a particular configuration, if a change in I_{CQ} fails to produce a significant change in I_C , the stability factor defined

by $S(I_{CQ}) = \frac{\Delta I_C}{\Delta I_{CQ}}$ will be quite small.

Network that are quite stable and relatively insensitive to temperature variations have low stability factors.

Voltage divider bias :-

$$S(I_{co}) = (\beta + 1) \frac{1 + R_{th}/R_E}{(\beta + 1) + (R_{th}/R_E)}$$

R_E 20 मान 9 \rightarrow 18 \rightarrow 90
 R_{th} 20 मान 8 \rightarrow 16 \rightarrow 72
 7 \rightarrow 14 \rightarrow 56
 6 \rightarrow 12 \rightarrow 42

Fixed - Bias Config. :-

$$S(I_{co}) = \beta + 1$$

3 \rightarrow 10 \rightarrow 32
 4 \rightarrow 8 \rightarrow 24
 3 \rightarrow 6 \rightarrow 18

Feedback - Bias Config. :-

$$S(I_{co}) = (\beta + 1) \frac{(1 + R_B/R_E)}{(\beta + 1) + R_B/R_E} \quad (4.6)$$

Construction & Characteristics of JFETs :-

Voltage Control Resistor :-

$$r_d = \frac{r_0}{(1 - V_{GS}/V_P)^2} \quad (5.1)$$

where, r_0 is the resistance with $V_{GS} = 0V$


r_d = The resistance at a particular level of V_{GS} .

P - Channel Devices :-

Graph of I_D vs V_{GS} Graph:-

Shorthand Method:-

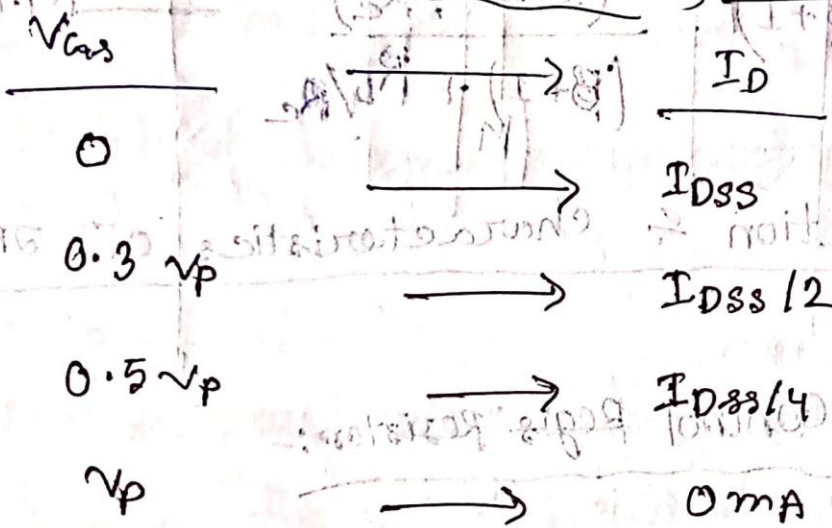
V_{GS} versus I_D using Shockley's Equation



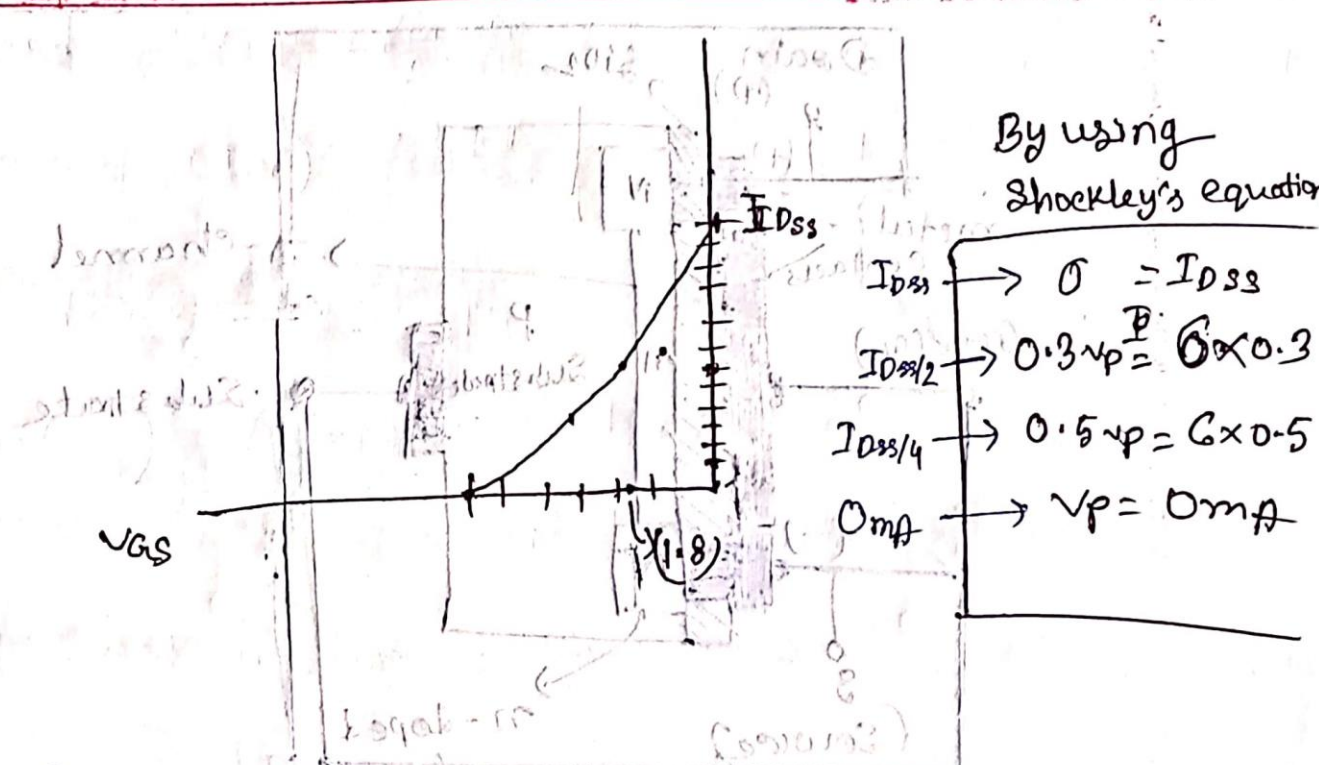Example:- Sketch the Transfer curve defined by $I_{DSS} = 12 \text{ mA}$ and $V_p = -6 \text{ V}$.

Solution:-

$I_{DSS} = 12 \text{ mA}$ and $V_{GS} = 0 \text{ V}$



Depletion Type MOSFET :-

MOSFETs are further broken down into depletion type and enhancement type.

The terms depletion and enhancement define their basic mode of operation.

MOSFET stands for Metal-Oxide-Semiconductor Field-effect transistor. Since there are differences in the characteristics and operation of each type of MOSFET, they are covered in separate sections.


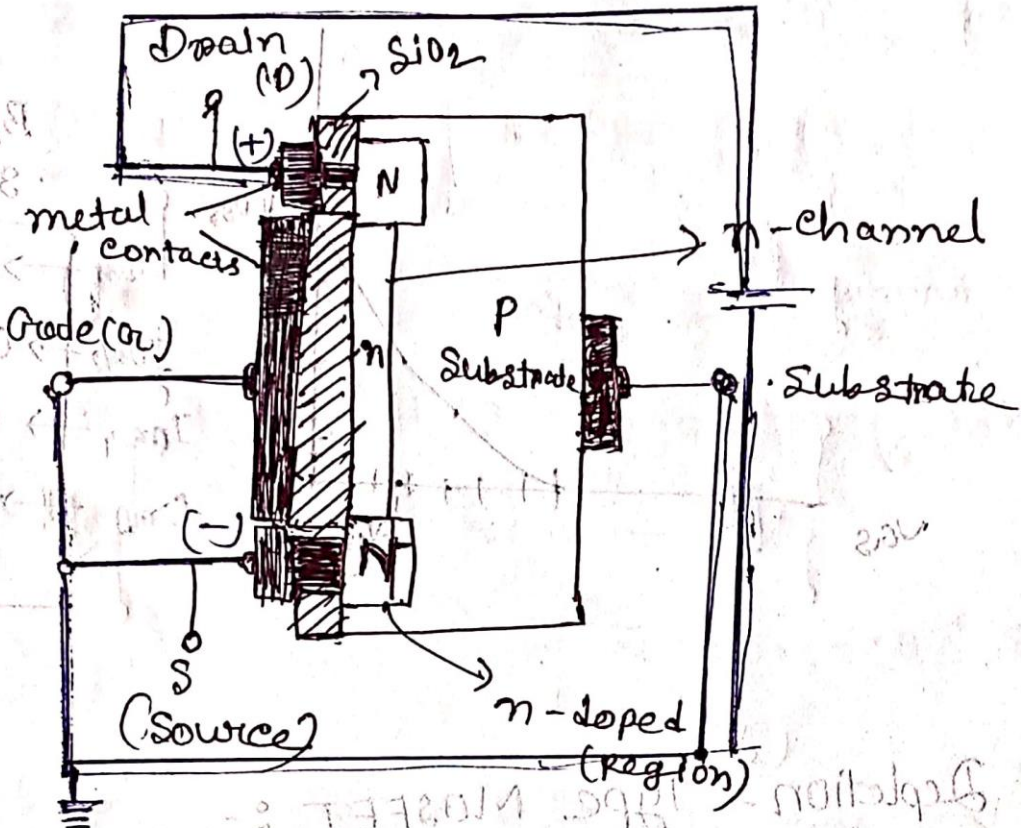


Figure: n-channel depletion type MOSFET

metal contacts বসানোর কারণে ড্রেন ও সোর্স-
 Metals দুমকে metallic লেভে connect করা
 হয়েছে।

=> N channel ও gate এর মাঝে SiO_2 এর
 একটি layer থাকে। একারণে একে oxide বলে।

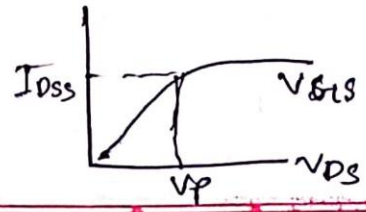=> এটি একটি semiconductor device ও
 => আমরা এখানে দেওয়া voltage এর সাথে drain
 current এর কোনো সংসর্গ নেই একারণে এটি



Field Effect Transistor বলে।

উদাহরণ স্বরূপে (MOSFET) এর।

operation of MOSFET (কাজ):-

উদাহরণ Figure এ (+) terminal n-type এর electron সুলোকে আকর্ষণ এবং (-) terminal electron সুলোকে ঠিক করা দিবে এর ফলে electron flow এর একটি পথ হবে।

voltage মত বাড়লে ohm's law অনুযায়ী electron flow বাড়বে। একসময় n-channel এর পরিবর্তন ঘটে যাবে। ফলে মতই voltage বাড়ানো হোক electron pass আর হবে না।

আর Negative যদি (Gate) এ দেওয়া হয় তখন বিকর্ষন তৈরি হয় electron-electron

MOSFET কে Depletion ^{type} region এ ব্যবহার করা হয়। যেহেতু সবসময় Depletion type এ ব্যবহার করা হয় তাই MOSFET কে Depletion Type Transistorও বলা হয়।


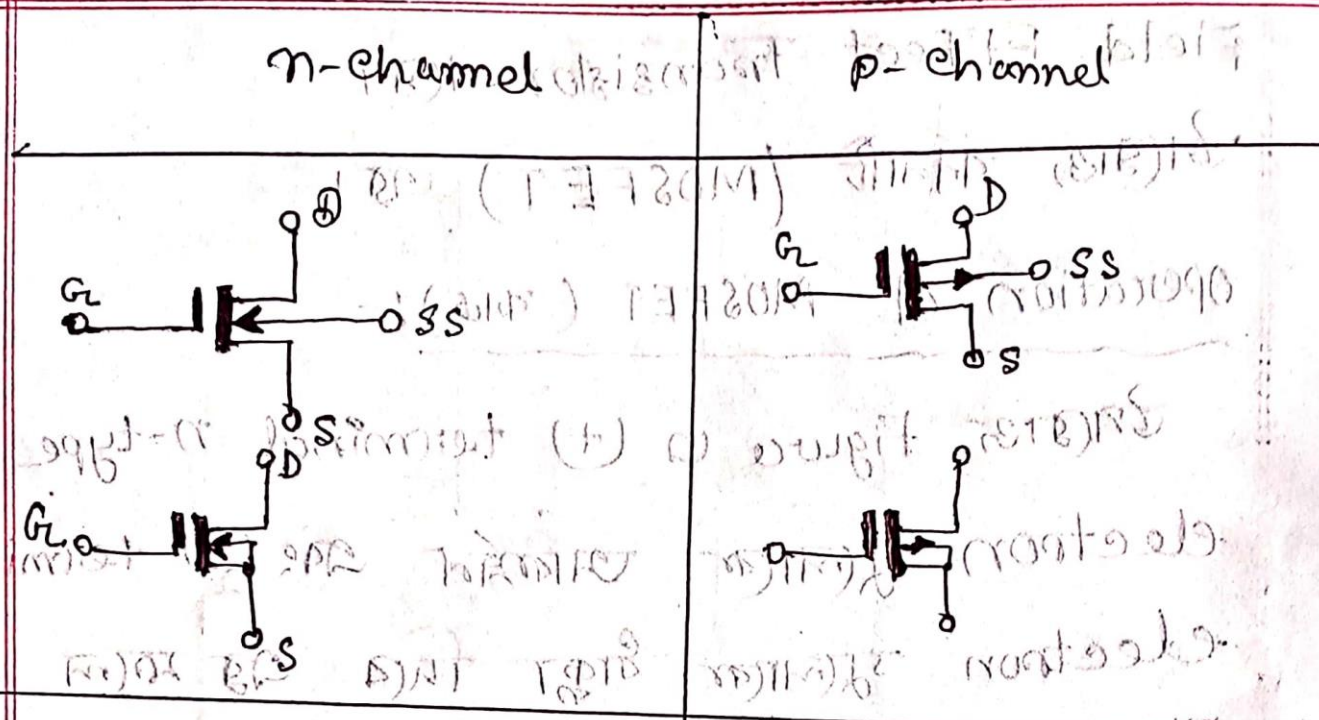


Figure:- Graphic Symbols for (a) n-channel depletion-type MOSFETs and (b) p-channel depletion-type MOSFETs

Enhancement MOSFET: $V_{IV} > V_{IN}$

এখানে কোম্পা n -channel ন্য।

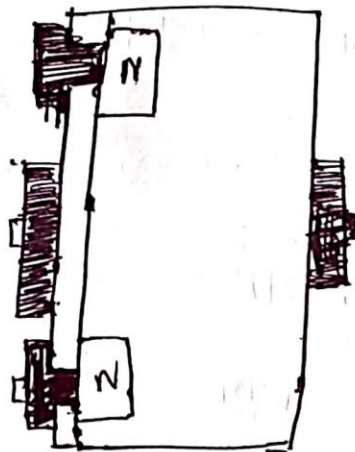

Question & answer:-

$$\begin{cases} V_{CE} = \frac{V_{CC} - I_c R_c}{\beta + 1} \\ I_c = \frac{V_{CC}}{R_c} \end{cases} \quad \beta = 80$$

$S(I_{co}) =$